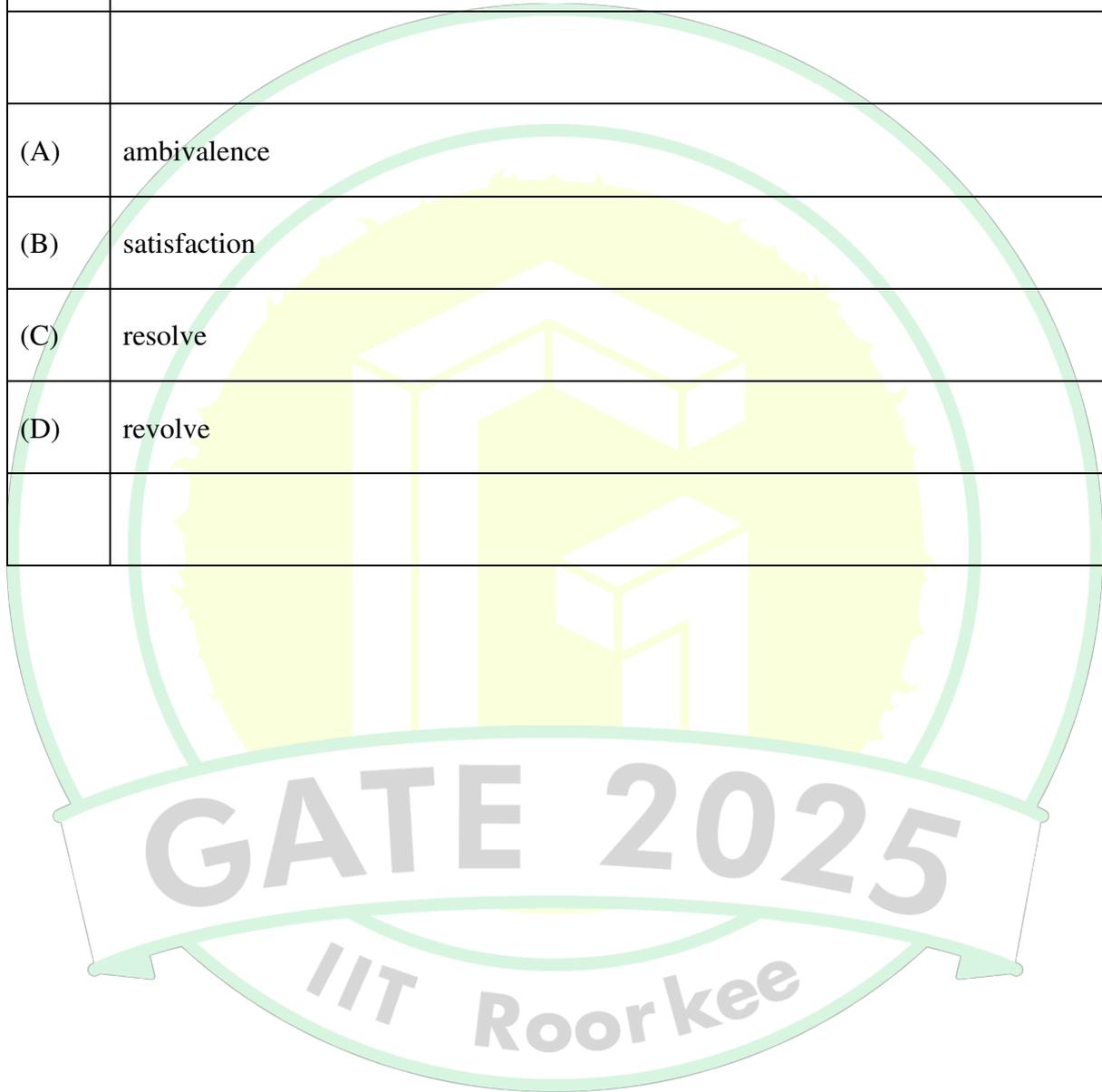




General Aptitude


Q.1 – Q.5 Carry ONE mark Each

Q.1	Despite his initial hesitation, Rehman’s _____ to contribute to the success of the project never wavered. Select the most appropriate option to complete the above sentence.
(A)	ambivalence
(B)	satisfaction
(C)	resolve
(D)	revolve










Q.2	Bird : Nest :: Bee : _____ Select the correct option to complete the analogy.
(A)	Kennel
(B)	Hammock
(C)	Hive
(D)	Lair

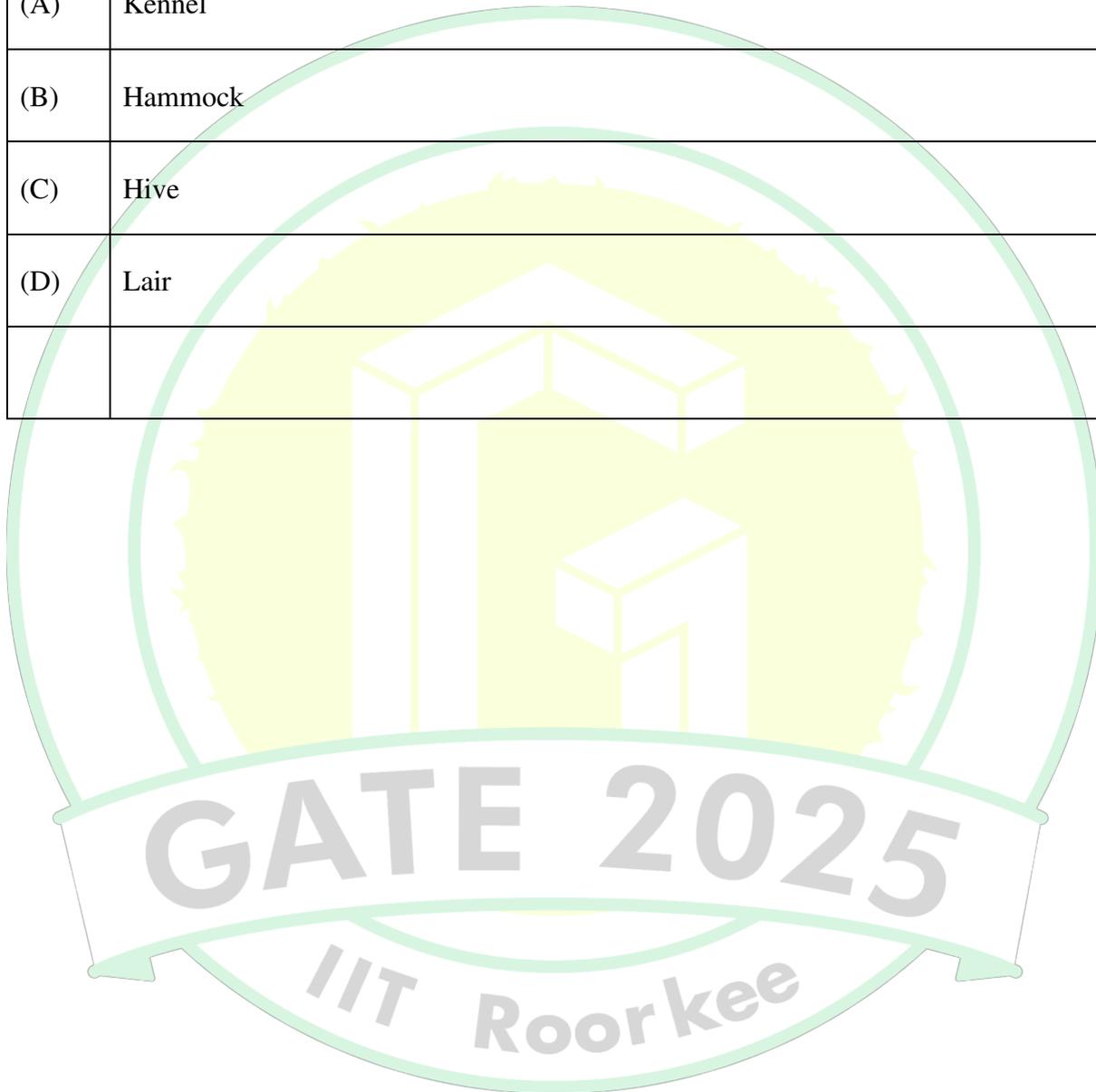



Q.3	If $Pe^x = Qe^{-x}$ for all real values of x , which one of the following statements is true?
(A)	$P = Q = 0$
(B)	$P = Q = 1$
(C)	$P = 1; Q = -1$
(D)	$\frac{P}{Q} = 0$

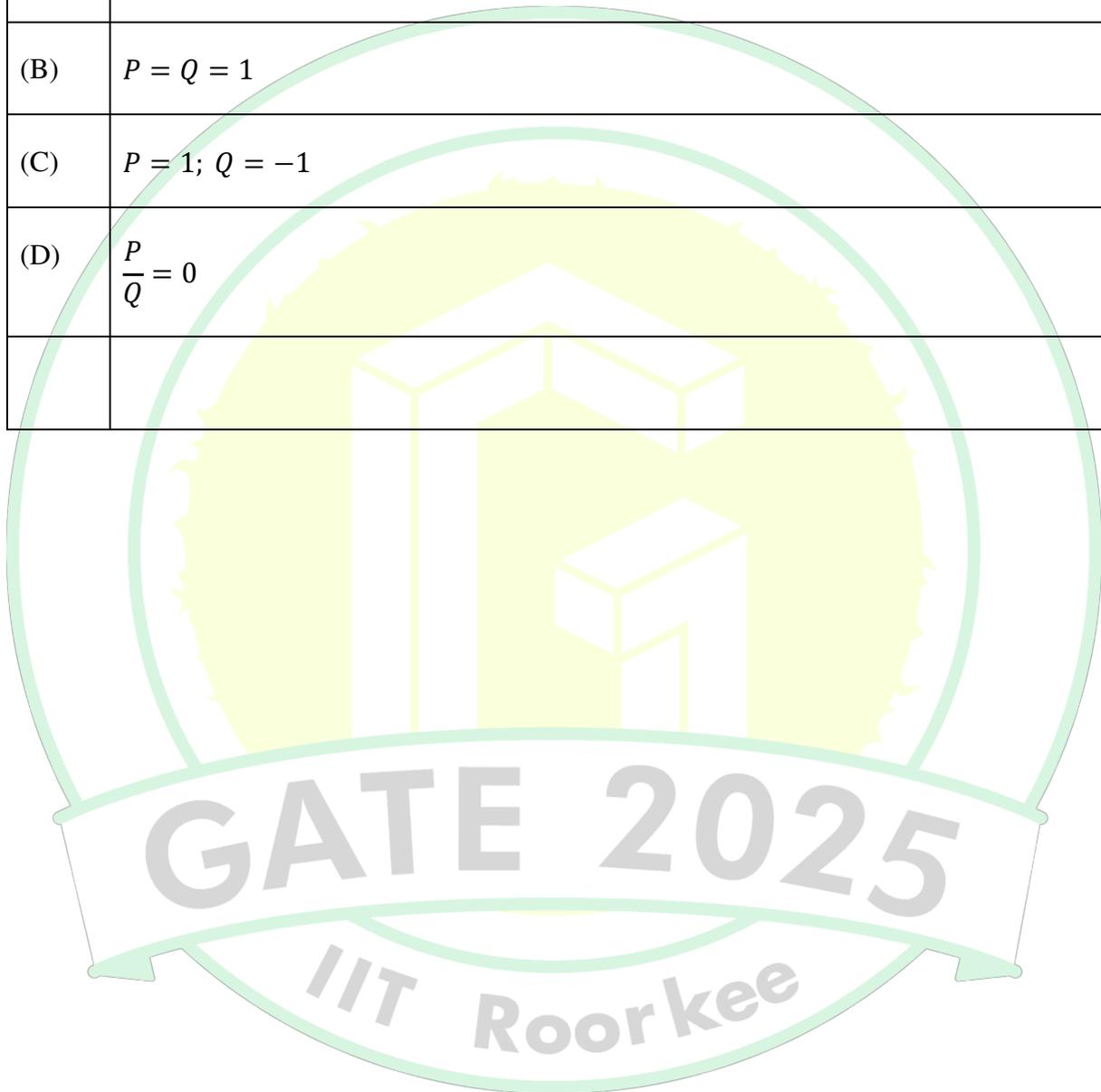

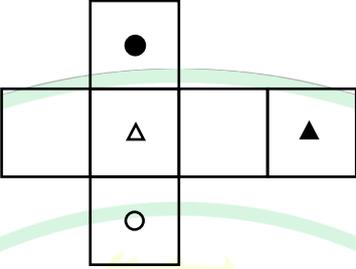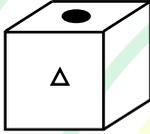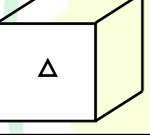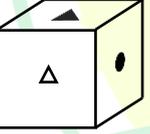
<p>Q.4</p>	<p>The paper as shown in the figure is folded to make a cube where each square corresponds to a particular face of the cube. Which one of the following options correctly represents the cube?</p> <p>Note: The figures shown are representative.</p>
	
<p>(A)</p>	
<p>(B)</p>	
<p>(C)</p>	
<p>(D)</p>	






Q.5	Let p_1 and p_2 denote two arbitrary prime numbers. Which one of the following statements is correct for all values of p_1 and p_2 ?
(A)	$p_1 + p_2$ is not a prime number.
(B)	$p_1 p_2$ is not a prime number.
(C)	$p_1 + p_2 + 1$ is a prime number.
(D)	$p_1 p_2 + 1$ is a prime number.

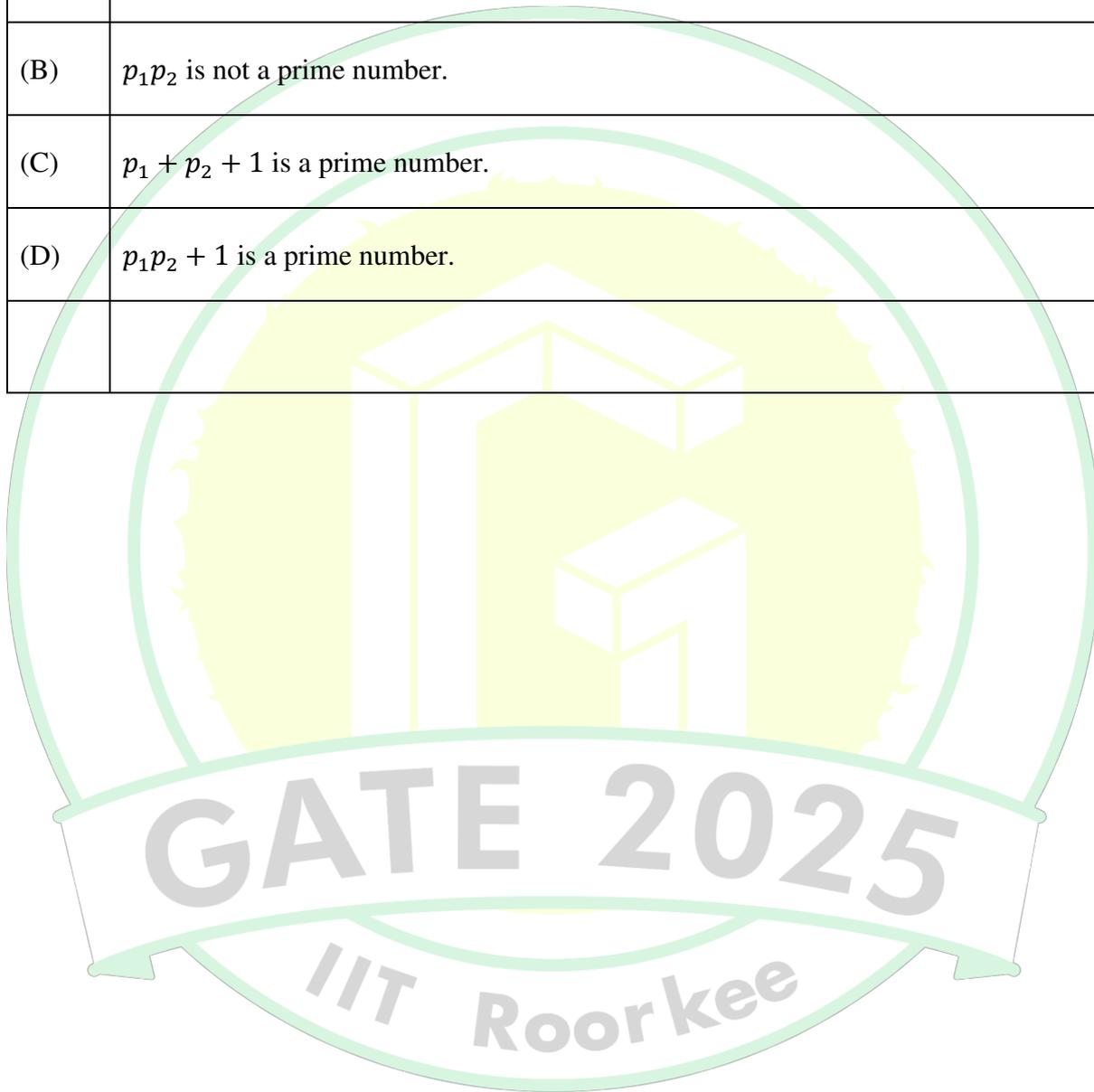




Q.6 – Q.10 Carry TWO marks Each

Q.6	Based only on the conversation below, identify the logically correct inference: “Even if I had known that you were in the hospital, I would not have gone there to see you”, Ramya told Josephine.
(A)	Ramya knew that Josephine was in the hospital.
(B)	Ramya did not know that Josephine was in the hospital.
(C)	Ramya and Josephine were once close friends; but now, they are not.
(D)	Josephine was in the hospital due to an injury to her leg.

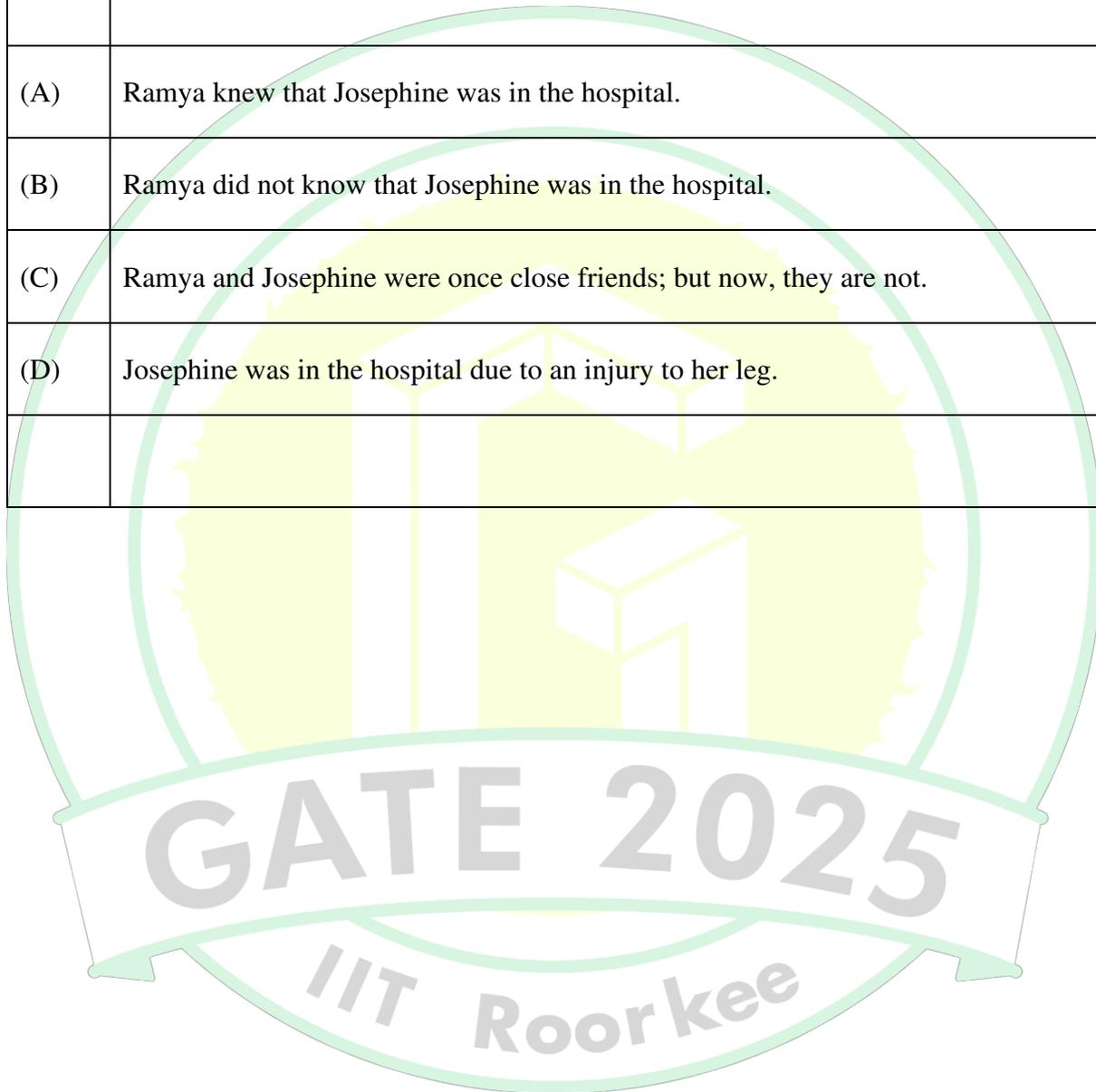



Q.7	If IMAGE and FIELD are coded as FHBNJ and EMFJG respectively then, which one among the given options is the most appropriate code for BEACH ?
(A)	CEADP
(B)	IDBFC
(C)	JGIBC
(D)	IBCEC

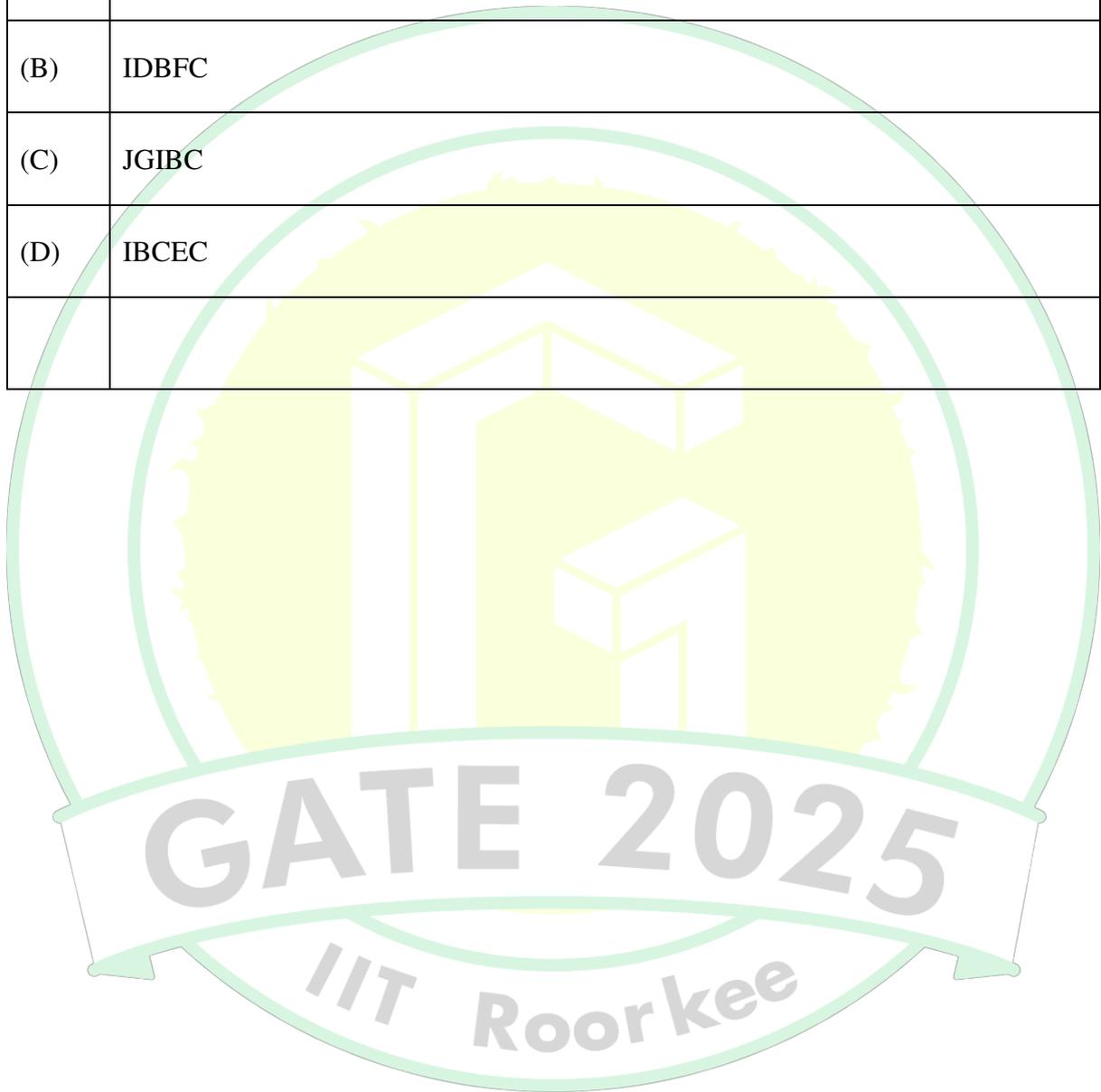


Q.8	Which one of the following options is correct for the given data in the table?																				
	<table border="1"> <tr> <td>Iteration (i)</td> <td>0</td> <td>1</td> <td>2</td> <td>3</td> </tr> <tr> <td>Input (I)</td> <td>20</td> <td>-4</td> <td>10</td> <td>15</td> </tr> <tr> <td>Output (X)</td> <td>20</td> <td>16</td> <td>26</td> <td>41</td> </tr> <tr> <td>Output (Y)</td> <td>20</td> <td>-80</td> <td>-800</td> <td>-12000</td> </tr> </table>	Iteration (i)	0	1	2	3	Input (I)	20	-4	10	15	Output (X)	20	16	26	41	Output (Y)	20	-80	-800	-12000
Iteration (i)	0	1	2	3																	
Input (I)	20	-4	10	15																	
Output (X)	20	16	26	41																	
Output (Y)	20	-80	-800	-12000																	
(A)	$X(i) = X(i - 1) + I(i); \quad Y(i) = Y(i - 1)I(i); \quad i > 0$																				
(B)	$X(i) = X(i - 1)I(i); \quad Y(i) = Y(i - 1) + I(i); \quad i > 0$																				
(C)	$X(i) = X(i - 1)I(i); \quad Y(i) = Y(i - 1)I(i); \quad i > 0$																				
(D)	$X(i) = X(i - 1) + I(i); \quad Y(i) = Y(i - 1)I(i - 1); \quad i > 0$																				



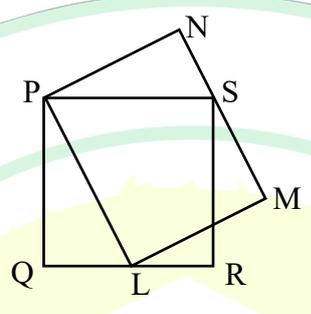
Q.9 In the given figure, PQRS is a square of side 2 cm and PLMN is a rectangle. The corner L of the rectangle is on the side QR. Side MN of the rectangle passes through the corner S of the square.

What is the area (in cm^2) of the rectangle PLMN?

Note: The figure shown is representative.




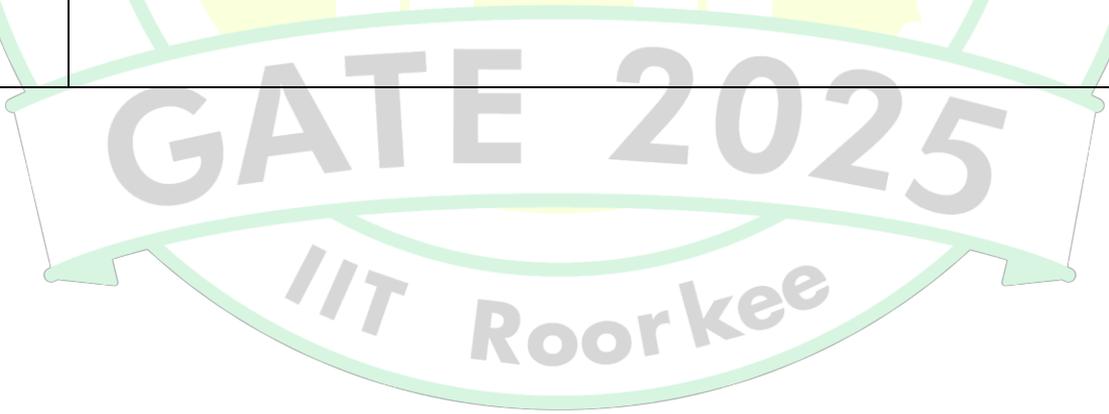- (A) $2\sqrt{2}$
- (B) 2
- (C) 8
- (D) 4



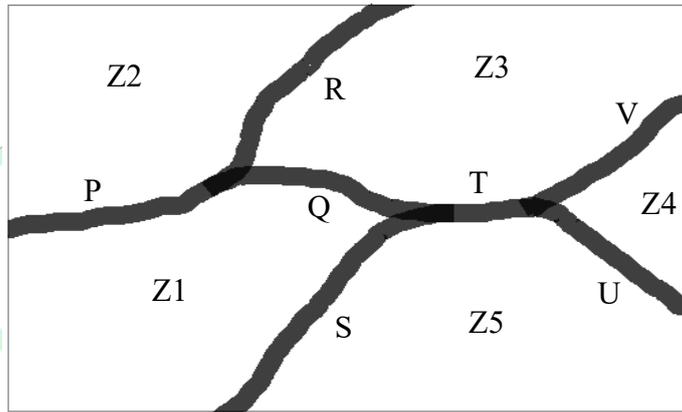Q.10 The diagram below shows a river system consisting of 7 segments, marked P, Q, R, S, T, U, and V. It splits the land into 5 zones, marked Z1, Z2, Z3, Z4, and Z5. We need to connect these zones using the least number of bridges. Out of the following options, which one is correct?

Note: The figure shown is representative.





- (A) Bridges on P, Q, and T
- (B) Bridges on P, Q, S, and T
- (C) Bridges on Q, R, T, and V
- (D) Bridges on P, Q, S, U, and V




Q.11 – Q.35 Carry ONE mark Each

Q.11	<p>A $2n \times 2n$ matrix $A = [a_{ij}]$ has its elements as</p> $a_{ij} = \begin{cases} \beta & \text{if } (i+j) \text{ is odd,} \\ -\beta & \text{if } (i+j) \text{ is even,} \end{cases}$ <p>where n is any integer greater than 2 and β is any non-zero real number. The rank of A is</p>
(A)	1
(B)	2
(C)	n
(D)	$2n$

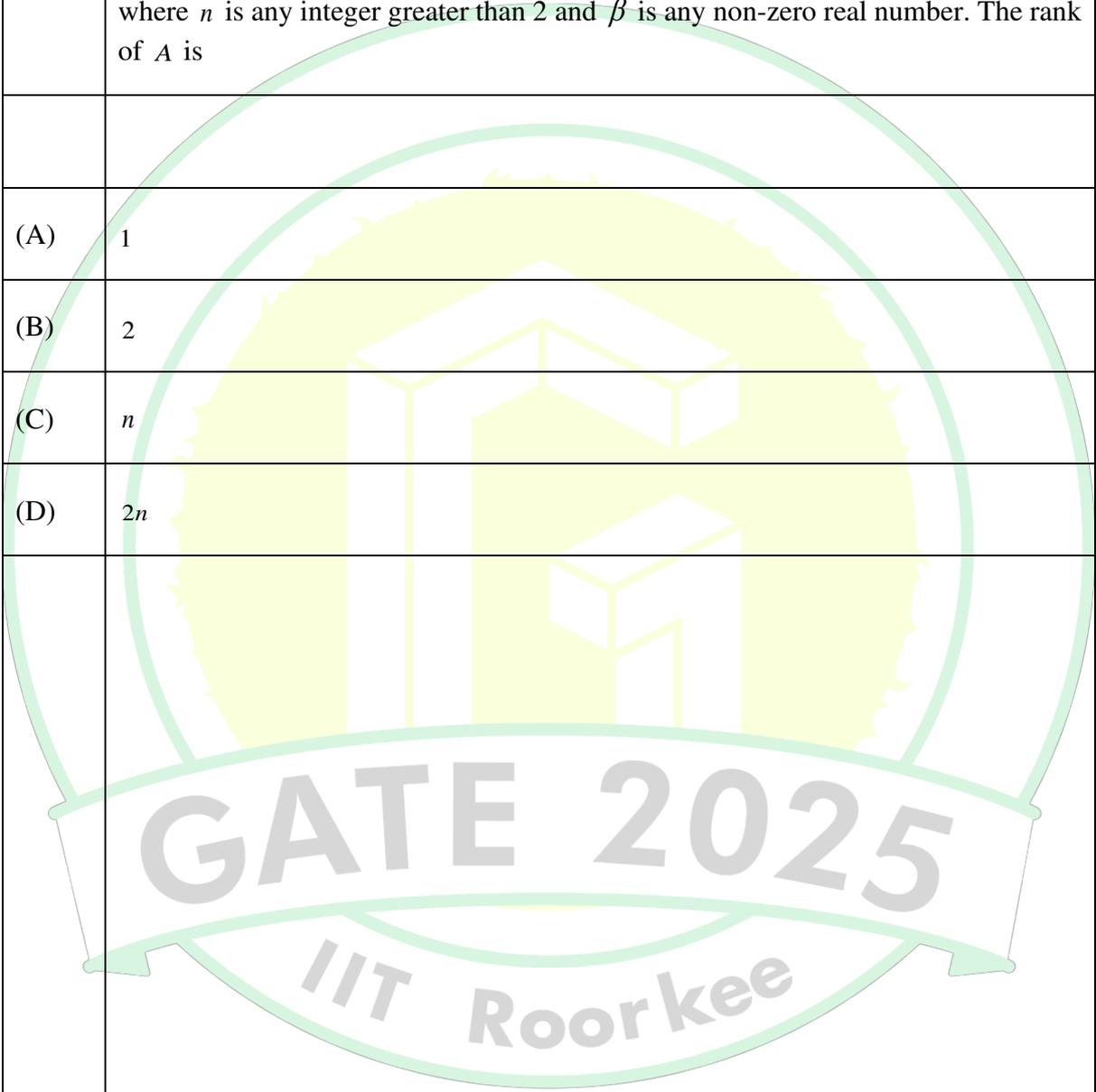

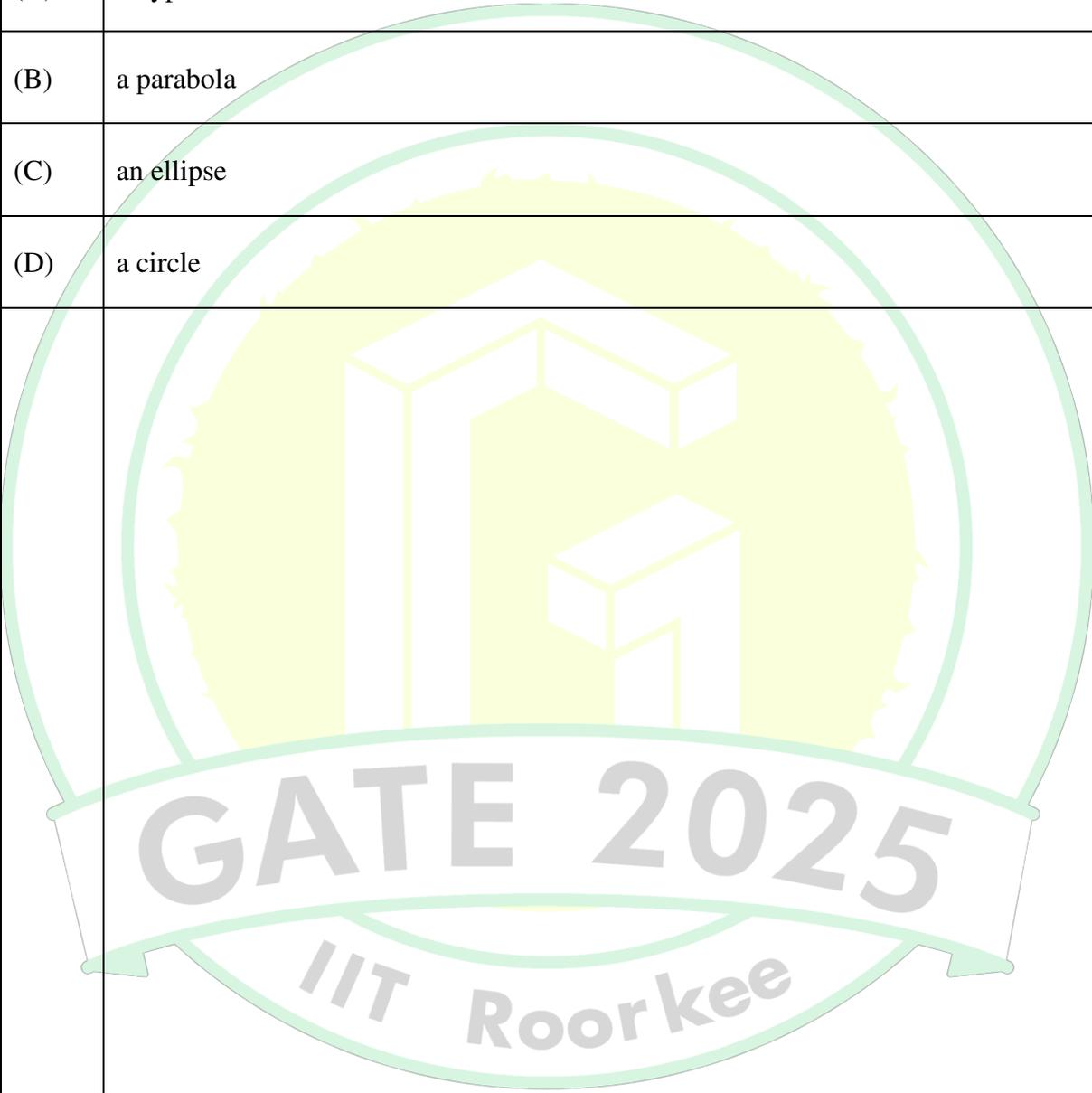
Q.12	The solution of the differential equation $\frac{dy}{dx} = 9\frac{x}{y}$ represents
(A)	a hyperbola
(B)	a parabola
(C)	an ellipse
(D)	a circle
	

Q.13	The working of the hand-held metal detector most widely used by security personnel for human frisking is based on the principle of
(A)	change in reluctance of an iron core in presence of a metallic object
(B)	change in conductance of an iron core in presence of a metallic object
(C)	electric field induced by a metallic object
(D)	eddy current generation in a metallic object

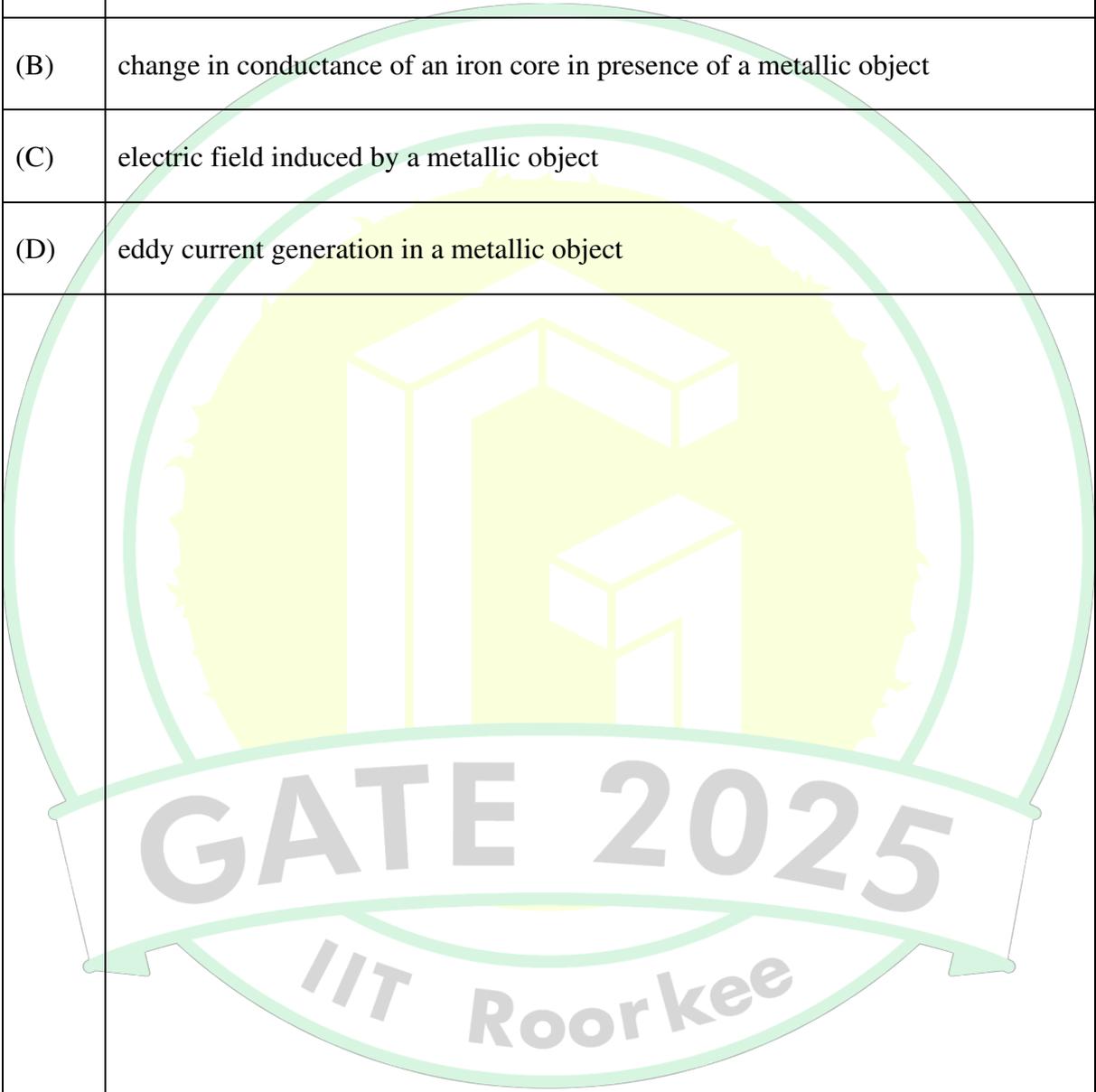

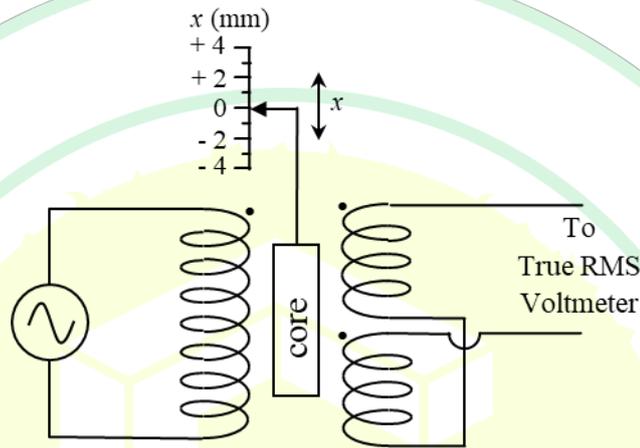Q.14

The primary coil of a linear variable differential transformer (LVDT) is supplied with AC voltage as shown in the figure. The secondary coils are connected in series opposition and the output is measured using a true RMS voltmeter. The displacement x of the core is indicated in mm on a linear scale. At the null position $x = 0$, the voltmeter reads 0 V. If the voltmeter reads 0.2 V for a displacement of $x = +2$ mm, then for a displacement of $x = -3$ mm, the voltmeter reading, in V, is



(A) - 0.3

(B) - 0.1

(C) 0.3

(D) 0.5

GATE 2025
IIT Roorkee

Q.15 In the force transducer shown in Figure (a), four identical strain gauges S1, S2, S3, and S4 are mounted on a cantilever at equal distance from its base. S1 and S2 are mounted on the top surface and S3 and S4 are mounted on the bottom surface, as shown in the Figure (a). These strain gauges are to be connected to form a Wheatstone bridge consisting of four arms A, B, C, and D, as shown in the Figure (b). From the following options, the correct order to maximize the measurement sensitivity is

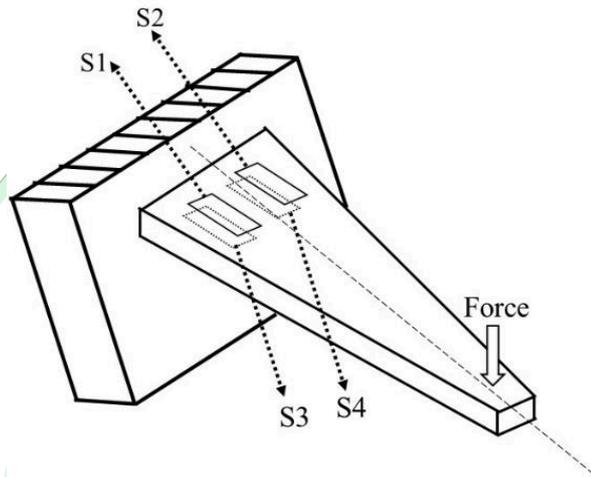


Figure (a)

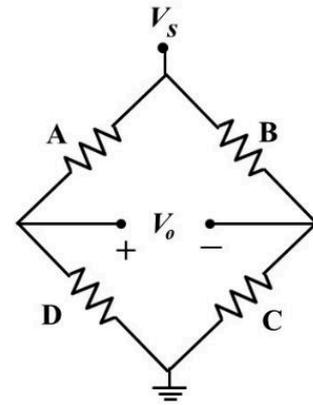


Figure (b)


(A) $A \rightarrow S1, B \rightarrow S2, C \rightarrow S4, D \rightarrow S3$

(B) $A \rightarrow S1, B \rightarrow S4, C \rightarrow S3, D \rightarrow S2$


(C) $A \rightarrow S1, B \rightarrow S2, C \rightarrow S3, D \rightarrow S4$

(D) $A \rightarrow S1, B \rightarrow S4, C \rightarrow S2, D \rightarrow S3$

Q.16	Let a continuous-time signal be $x(t) = e^{j9t} + e^{j5t}$, where $j = \sqrt{-1}$ and t is in seconds. The fundamental period of magnitude of $x(t)$, in seconds, is
(A)	π
(B)	$\frac{\pi}{2}$
(C)	$\frac{\pi}{5}$
(D)	$\frac{\pi}{9}$

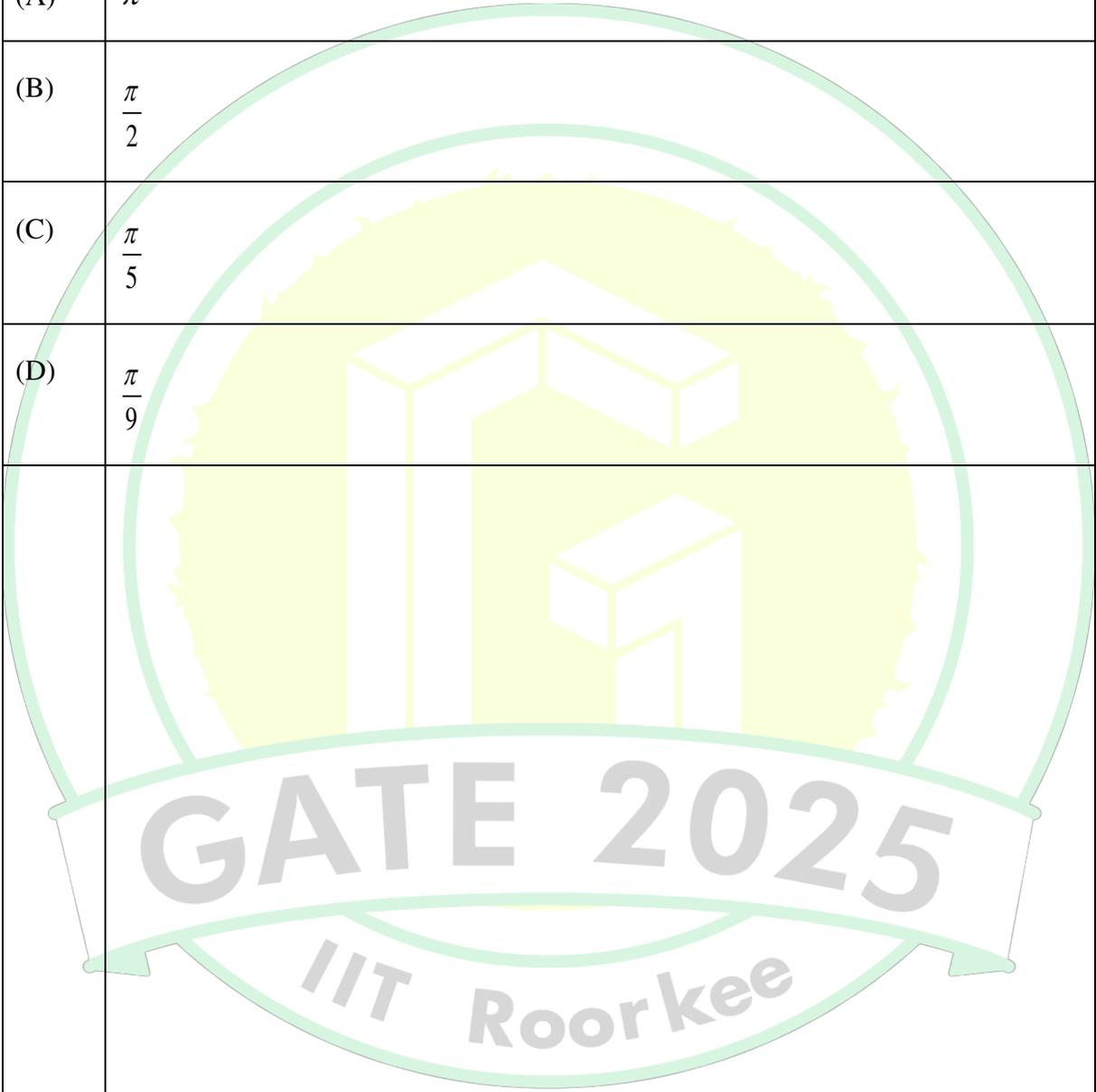

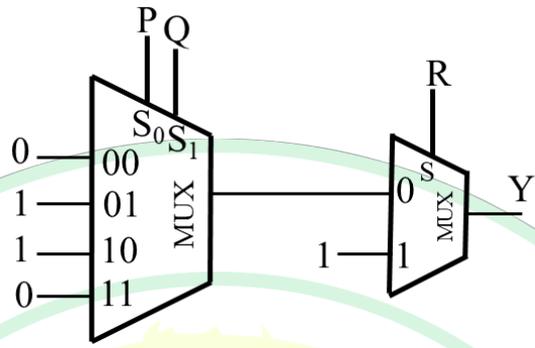Q.17 The minimized expression of the Boolean function $Y(P, Q, R)$ implemented by the multiplexer (MUX) circuit shown in the figure is





- (A) $Y = R + (P \oplus Q)$
- (B) $Y = R (P \oplus Q)$
- (C) $Y = R + (\overline{P \oplus Q})$
- (D) $Y = R \oplus (P \oplus Q)$






Q.18	The 4-bit signed 2's complement form of $(5)_{10} + (5)_{10}$ is
(A)	$(-6)_{10}$
(B)	$(-7)_{10}$
(C)	$(-5)_{10}$
(D)	$(-8)_{10}$

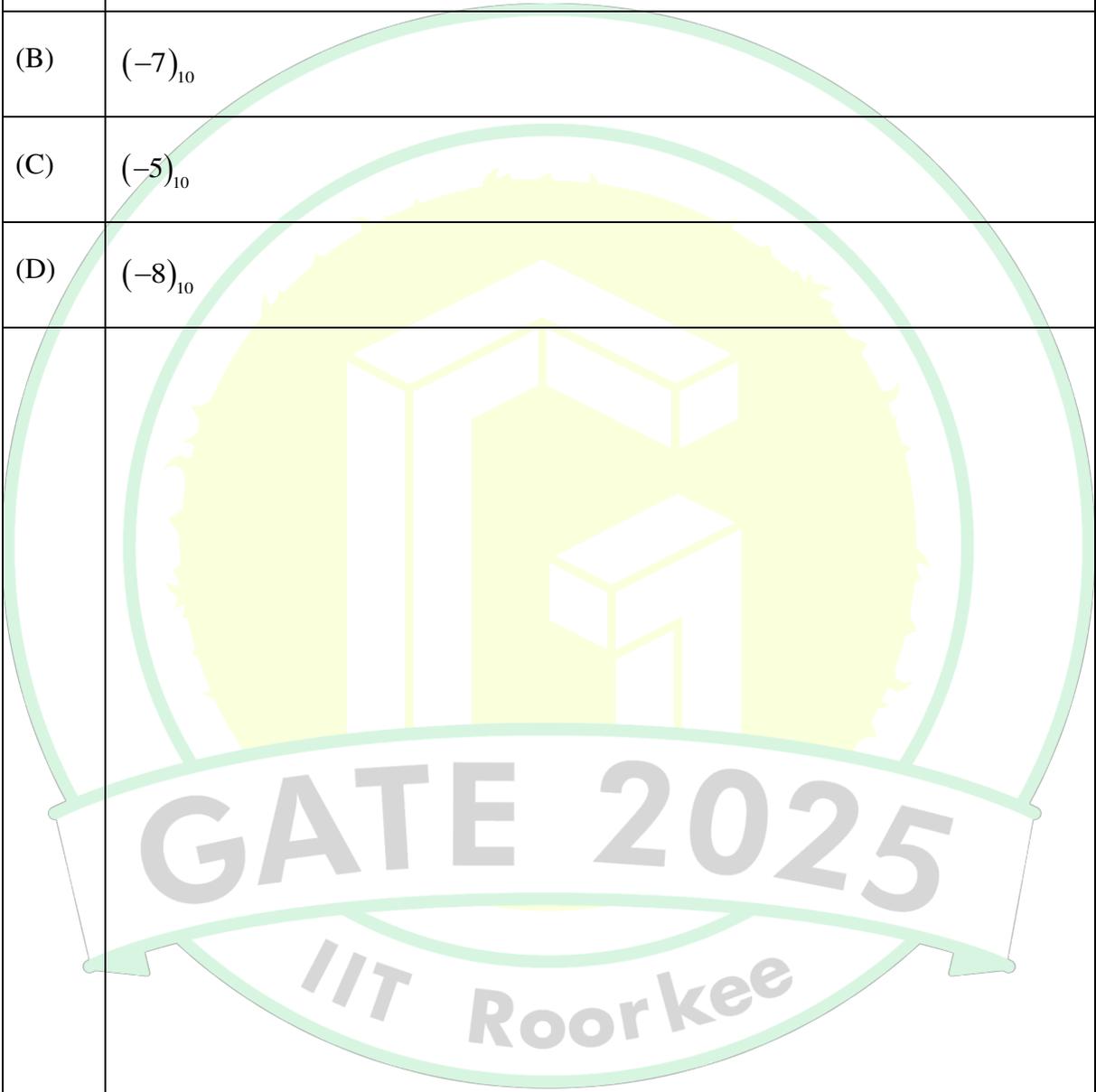

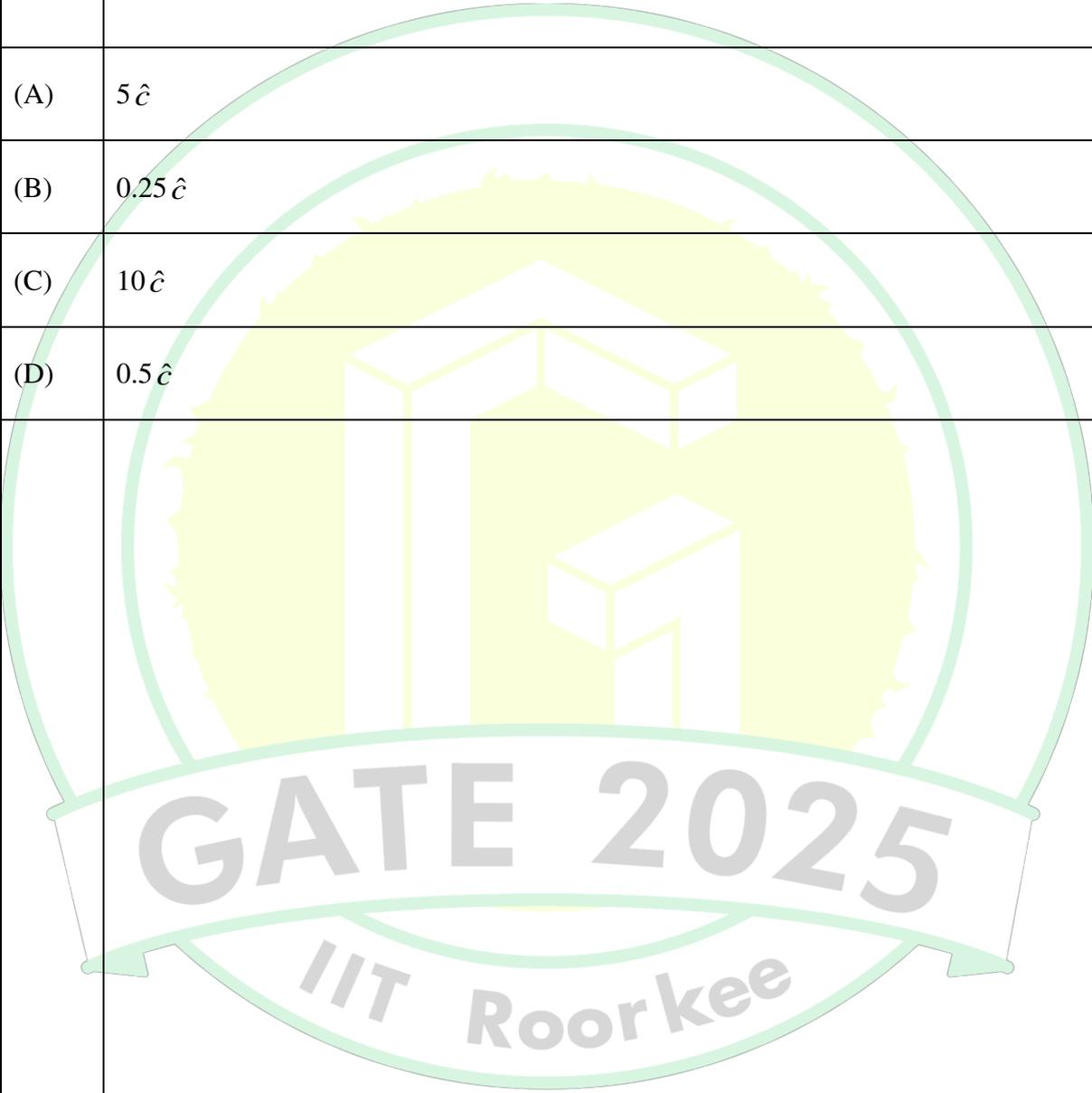Q.19	<p>An infinite sheet of uniform charge $\rho_s = 10 \text{ C/m}^2$ is placed on $z = 0$ plane. The medium surrounding the sheet has a relative permittivity of 10. The electric flux density, in C/m^2, at a point $P(0, 0, 5)$, is</p> <p>Note: \hat{a}, \hat{b}, and \hat{c} are unit vectors along the x, y, and z directions, respectively.</p>
(A)	$5 \hat{c}$
(B)	$0.25 \hat{c}$
(C)	$10 \hat{c}$
(D)	$0.5 \hat{c}$
	

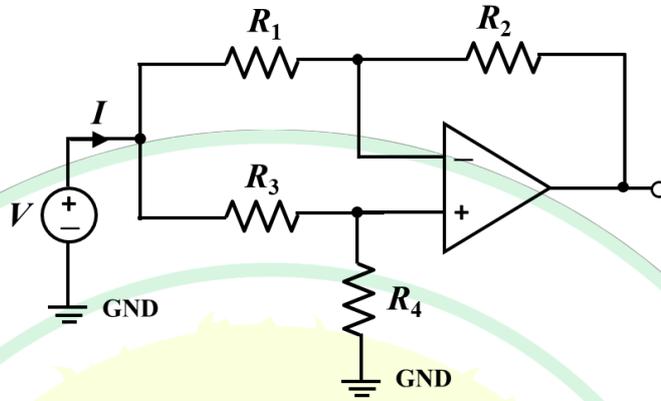Q.20

For the ideal opamp based circuit shown in the figure, the ratio $\frac{V}{I}$ is



(A)

$$\left(\frac{R_3 + R_4}{R_1 + R_3} \right) R_1$$

(B)

$$\left(\frac{R_2 + R_4}{R_1 + R_3} \right) R_3$$

(C)

$$R_1 + R_3$$


(D)

$$R_3 + R_4$$

GATE 2025

IIT Roorkee

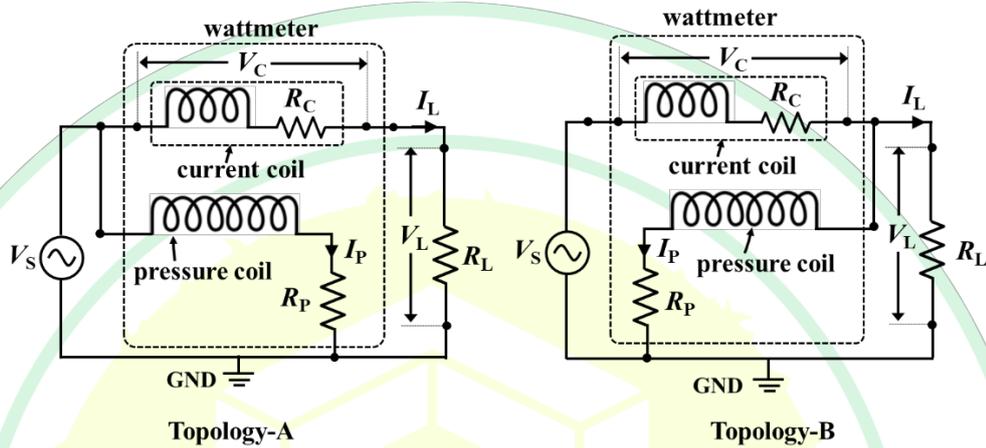Q.21 In a single-phase AC circuit, the power consumed by load resistance R_L for an excitation V_S is measured using a wattmeter. The same wattmeter is connected in two different topologies, Topology-A and Topology-B, as shown in the figure. Different branch currents and voltage drops are also marked in the figure. Among the following options, the condition that ensures low error in the wattmeter reading for both the topologies is



- (A) $V_L \gg V_C$ for Topology-A and $I_L \gg I_P$ for Topology-B
- (B) $V_L \gg V_C$ for Topology-A and $I_L \ll I_P$ for Topology-B
- (C) $V_L \ll V_C$ for Topology-A and $I_L \ll I_P$ for Topology-B
- (D) $V_L \ll V_C$ for Topology-A and $I_L \gg I_P$ for Topology-B

GATE 2025


IIT Roorkee

Q.22	Match the following sensors with their most suitable applications.			
	Sensor		Application	
	P	Rotary Variable Differential Transformer	I	Vacuum measurement
	Q	Thermocouple	II	Force measurement
	R	Ionization Gauge	III	Angular displacement measurement
	S	Strain Gauge	IV	Temperature measurement
(A)	P – II, Q – III, R – I, S – IV			
(B)	P – II, Q – IV, R – III, S – I			
(C)	P – III, Q – IV, R – II, S – I			
(D)	P – III, Q – IV, R – I, S – II			

Q.23	<p>A $3\frac{1}{2}$ digit digital voltmeter has a specified accuracy of $\pm(0.5\% + 1)$. If it is used to measure 10V DC voltage, the error in the measurement would be</p> <p>Note: Accuracy of the digital voltmeter is expressed as $\pm (\% \text{ of reading} + \text{digit})$.</p>
(A)	$\pm 0.4\%$
(B)	$\pm 1.5\%$
(C)	$\pm 0.6\%$
(D)	$\pm 1\%$
	

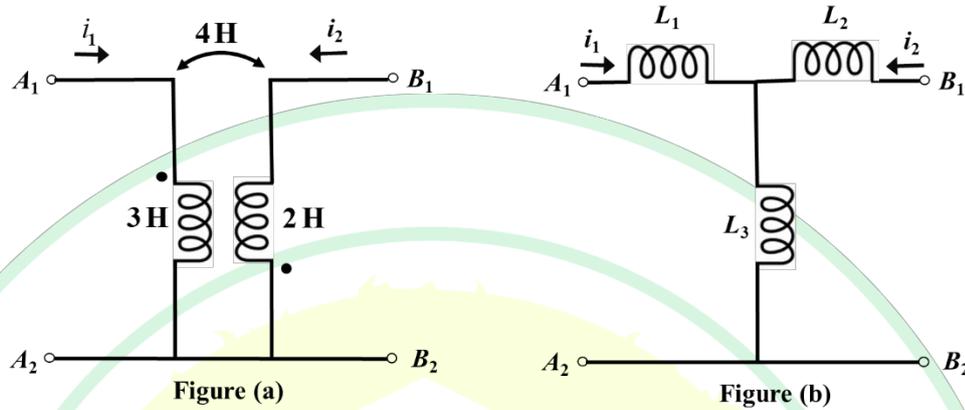Q.24

The circuit shown in Figure (a) can be represented using its equivalent T-model as shown in Figure (b). The values of the inductances L_1 , L_2 , and L_3 in the equivalent T-model are




- (A) $L_1 = 7\text{ H}, L_2 = 6\text{ H}, L_3 = -4\text{ H}$
- (B) $L_1 = -1\text{ H}, L_2 = -2\text{ H}, L_3 = 4\text{ H}$
- (C) $L_1 = 3\text{ H}, L_2 = 2\text{ H}, L_3 = 9\text{ H}$
- (D) $L_1 = 1\text{ H}, L_2 = -2\text{ H}, L_3 = -4\text{ H}$

GATE 2025

IIT Roorkee

Q.25	Three parallel admittances $Y_a = -j0.2 \text{ S}$, $Y_b = 0.3 \text{ S}$, and $Y_c = j0.4 \text{ S}$ connected in parallel with a voltage source $V_s = 10\angle 45^\circ \text{ V}$, draw a total current I_s from the source. The currents flowing through each of these admittances are I_a , I_b , and I_c , respectively. Let $I = I_b + I_c$. The phase relation between I and I_s is
(A)	I leads I_s by 19.44°
(B)	I lags I_s by 19.44°
(C)	I leads I_s by 33.69°
(D)	I lags I_s by 33.69°

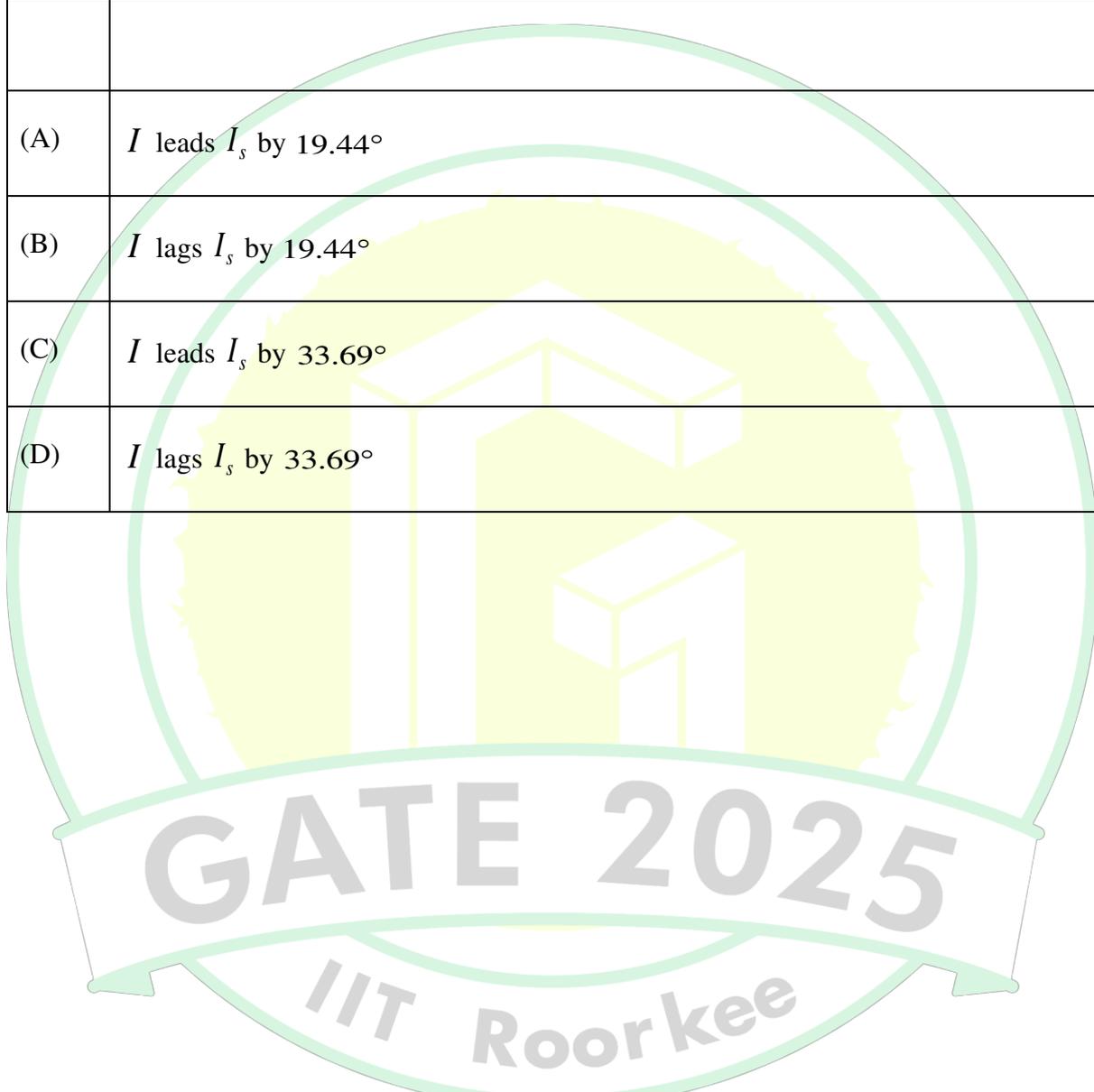


GATE 2025



IIT Roorkee

Q.26	An oscilloscope has an input resistance of $1\text{ M}\Omega$. A 10X passive attenuating probe is connected to it to increase the input voltage range as well as the effective input resistance. The effective input resistance, in $\text{M}\Omega$, seen into the probe tip is
(A)	0.9
(B)	9.1
(C)	10
(D)	11
	



Q.27	For the transfer function $G(s) = 1 + \frac{2s-1}{s^3 + 5s^2 + 3s + 22}$, the number of zeros lying in the left half of the s -plane is
(A)	0
(B)	1
(C)	2
(D)	3

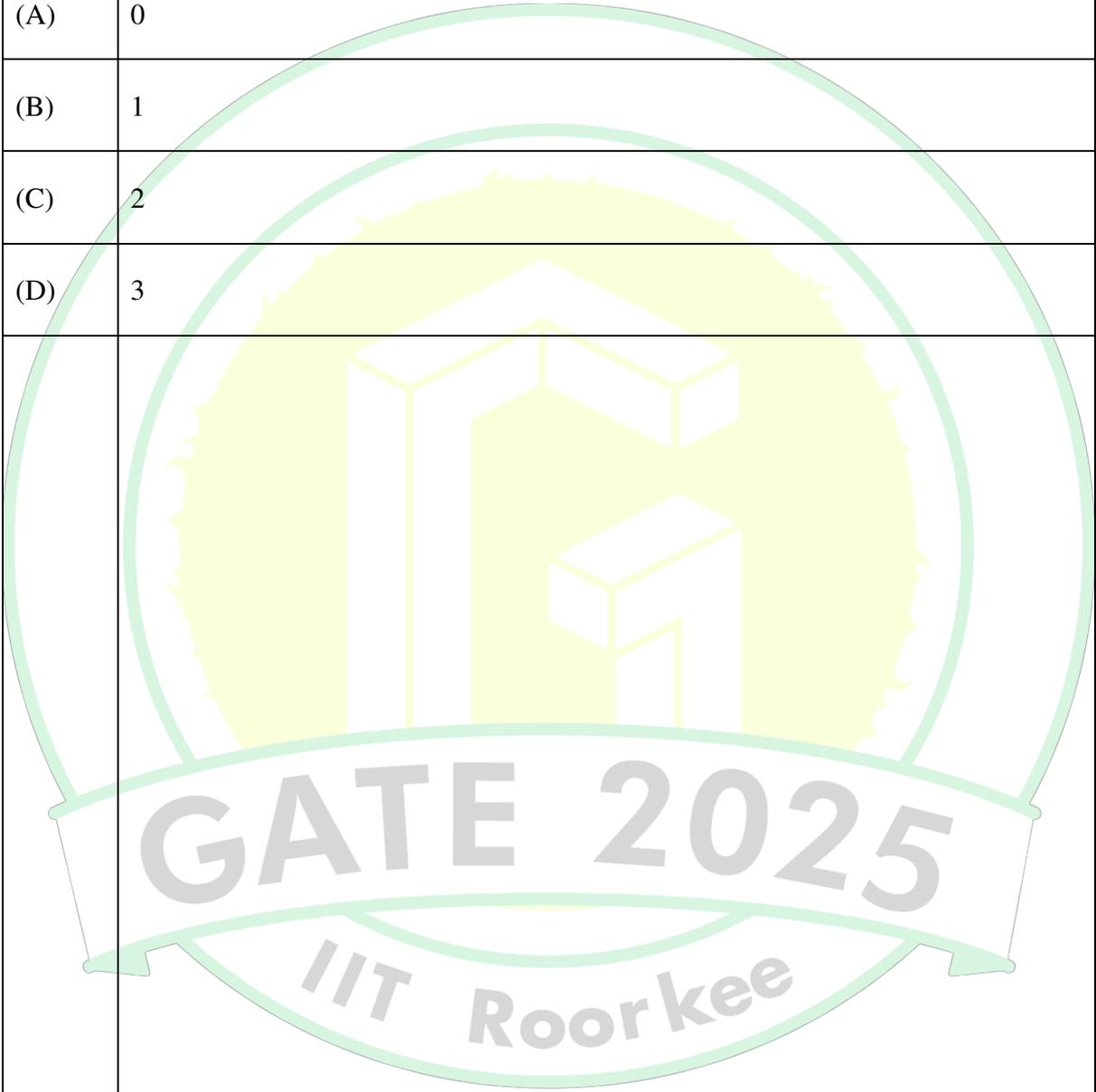
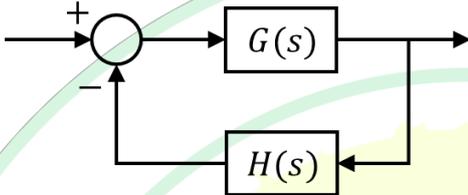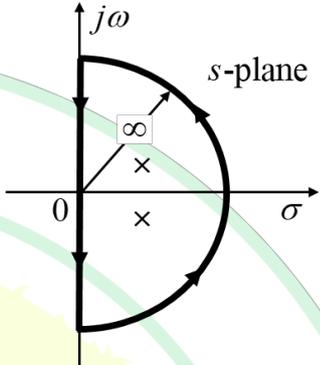
<p>Q.28</p>	<p>Consider the control system block diagram given in Figure (a). The loop transfer function $G(s)H(s)$ does not have any pole on the $j\omega$-axis. The counterclockwise contour with infinite radius, as shown in Figure (b), encircles two poles of $G(s)H(s)$. Choose the correct statement from the following options for closed loop stability of the system.</p>
	<div style="display: flex; justify-content: space-around; align-items: center;"> <div style="text-align: center;">  <p>Figure (a)</p> </div> <div style="text-align: center;">  <p>Figure (b)</p> <p>× : Poles encircled by the contour</p> </div> </div>
<p>(A)</p>	<p>The locus of $G(s)H(s)$ should encircle the origin twice in the counterclockwise direction</p>
<p>(B)</p>	<p>The locus of $1+G(s)H(s)$ should encircle the origin twice in the clockwise direction</p>
<p>(C)</p>	<p>The locus of $G(s)H(s)$ should encircle the $-1+j0$ point twice in the counterclockwise direction</p>
<p>(D)</p>	<p>The locus of $1+G(s)H(s)$ should encircle the $-1+j0$ point twice in the clockwise direction</p>




Q.29	A Boolean function X is given as $X = \bar{A}\bar{B} + \bar{A}\bar{C}$. The reduced form of \bar{X} is
(A)	$\bar{A} + \bar{B} + \bar{C}$
(B)	$A + BC$
(C)	$\bar{A} + \bar{B} + C$
(D)	$B + AC$

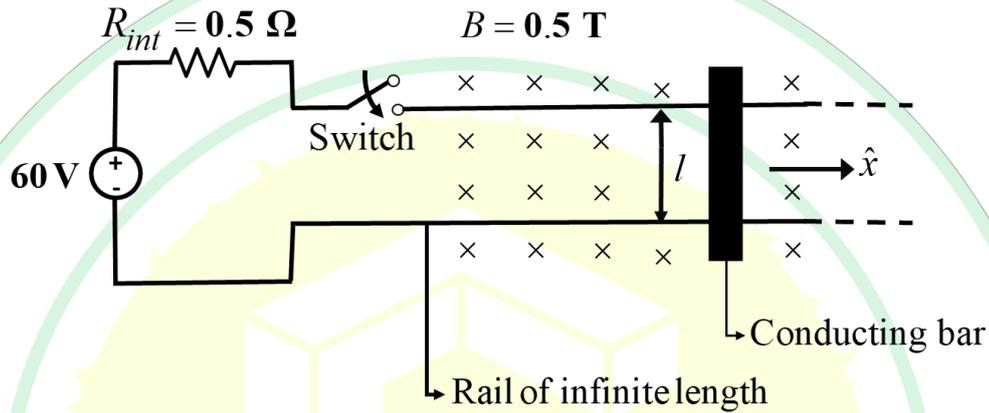Q.30

A 60 V DC source with an internal resistance $R_{int} = 0.5 \Omega$ is connected through a switch to a pair of infinitely long rails separated by $l = 1 \text{ m}$ as shown in the figure. The rails are placed in a constant, uniform magnetic field of flux density $B = 0.5 \text{ T}$, directed into the page. A conducting bar placed on these rails is free to move. At the instant of closing the switch, the force induced on the bar is

Note: Assume there is no friction between the bar and the rails. The resistances of the conducting bar and the rails are zero.



- (A) 60 N in the direction of \hat{x}
- (B) 60 N opposite to the direction of \hat{x}
- (C) 120 N in the direction of \hat{x}
- (D) 120 N opposite to the direction of \hat{x}

Q.32

If one of the eigenvectors of the matrix $A = \begin{bmatrix} -1 & -1 \\ x & -4 \end{bmatrix}$ is along the direction of $\begin{bmatrix} \alpha \\ 2\alpha \end{bmatrix}$, where α is any non-zero real number, then the value of x is _____ (in integer).



Q.33

Consider the function $f(z) = \frac{2z+1}{z^2-z}$, where z is a complex variable.

The sum of the residues at singular points of $f(z)$ is _____ (in integer).






Q.34

A dual-slope ADC has a fixed integration time of 100 ms. The reference voltage of the ADC is -5 V. The time taken by the ADC to measure an input voltage of 1.25 V is _____ ms (**rounded off to the nearest integer**).



Q.35

In the circuit shown, assume that the BJT in the circuit has very high β and $V_{BE} = 0.7 \text{ V}$, and the Zener diode has $V_Z = 4.7 \text{ V}$. The current I through the LED is _____ mA (rounded off to two decimal places).

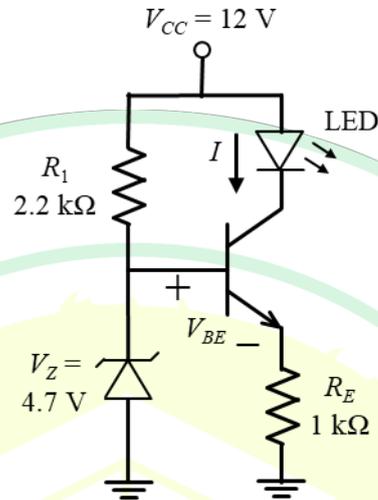


GATE 2025

IIT Roorkee

Q.36 – Q.65 Carry TWO marks Each


Q.36	The value of the surface integral $\iint_S (2x+z)dy dz + (2x+z)dx dz + (2z+y)dx dy$ over the sphere $S: x^2 + y^2 + z^2 = 9$ is
(A)	72π
(B)	144π
(C)	36π
(D)	432π

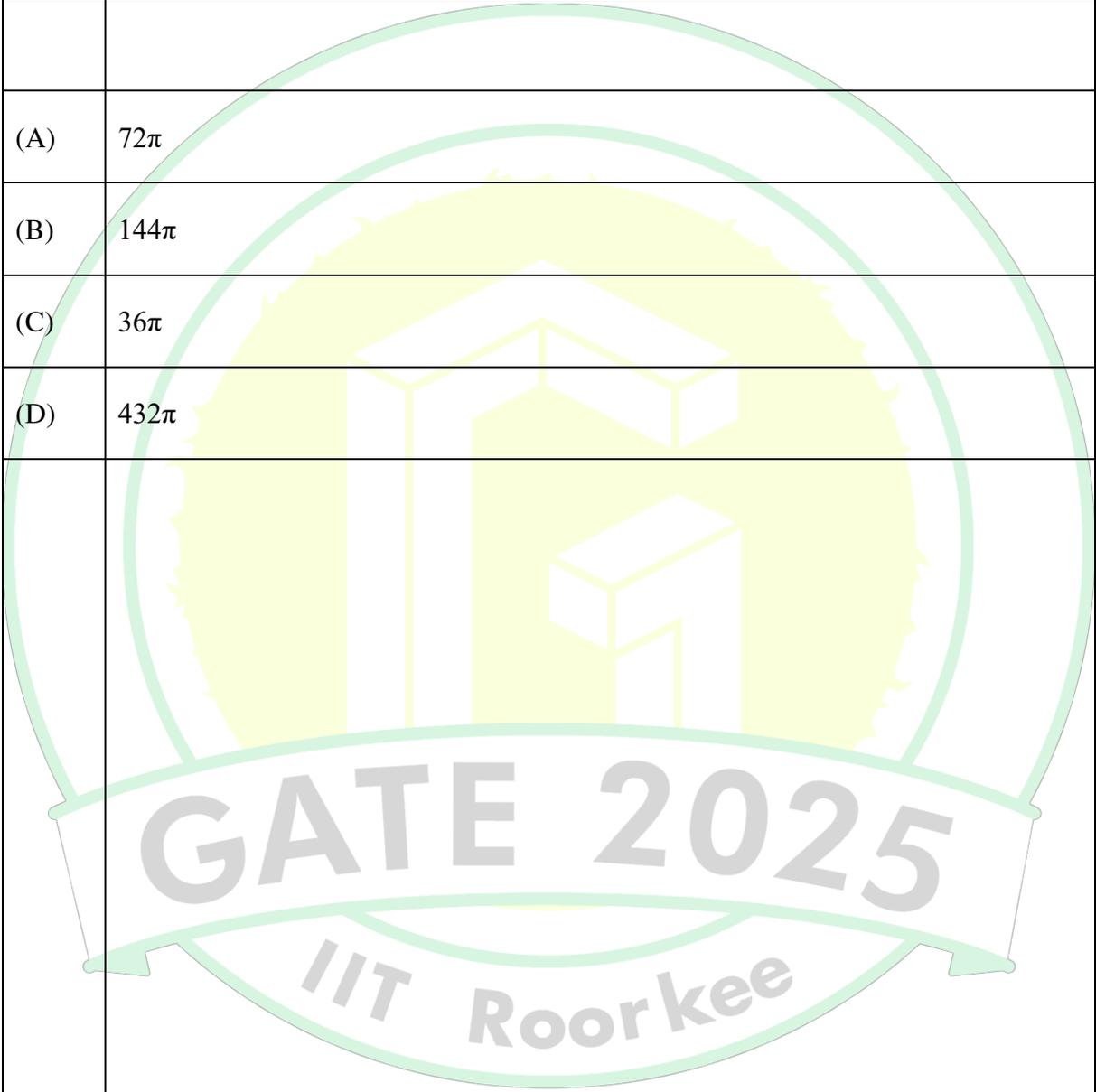




Q.37	Newton-Raphson method is used to compute the inverse of the number 1.6. Among the following options, the initial guess of the solution that results in non-convergence of the iterative process is
(A)	0.55
(B)	0.75
(C)	1.15
(D)	1.25

Q.38	The value of the integral $\int_{-\pi}^{\pi} (\cos^6 x + \cos^4 x) dx$ is
(A)	$\frac{\pi}{2}$
(B)	$\frac{5\pi}{8}$
(C)	$\frac{11\pi}{8}$
(D)	$\frac{9\pi}{8}$

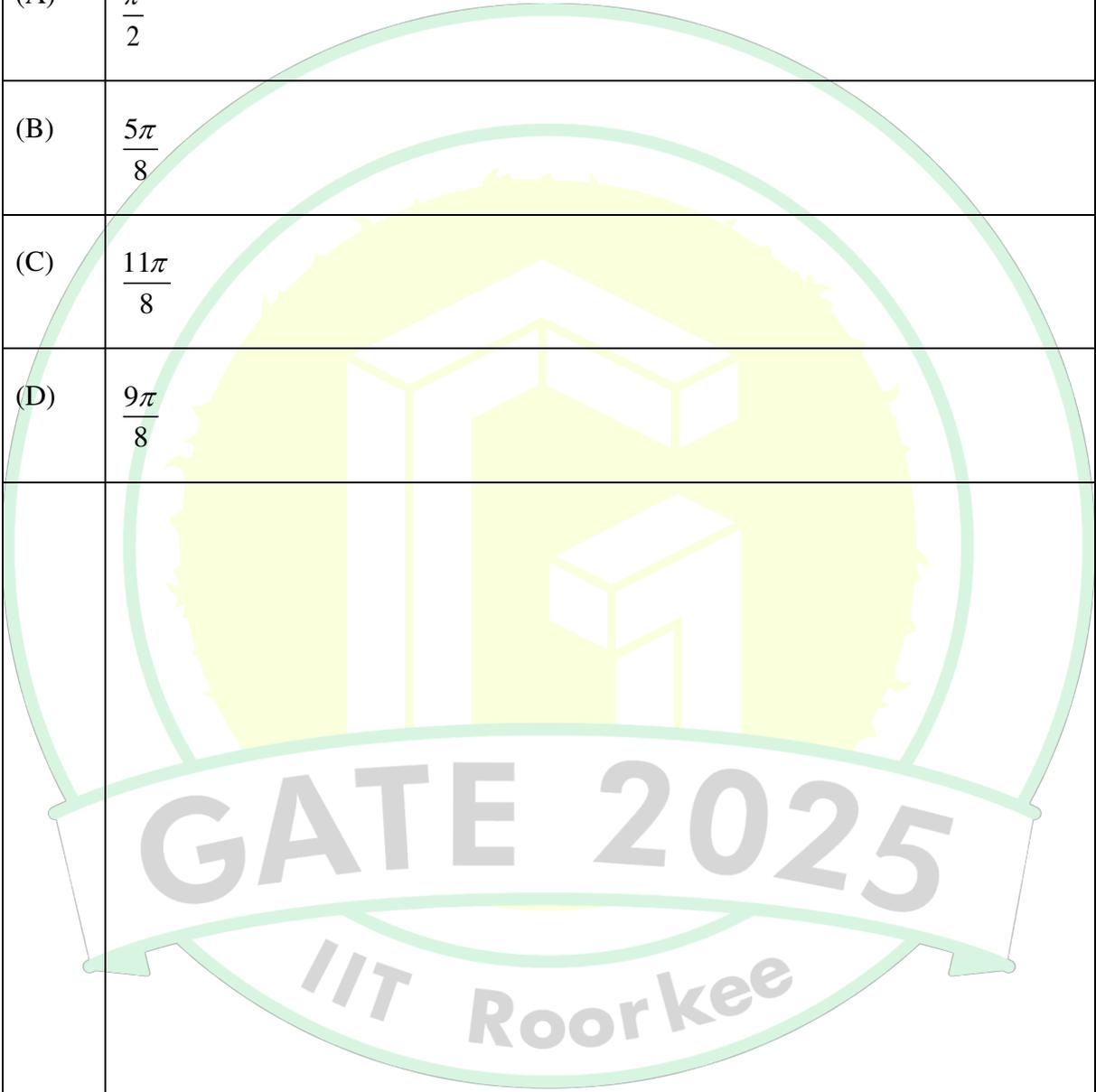

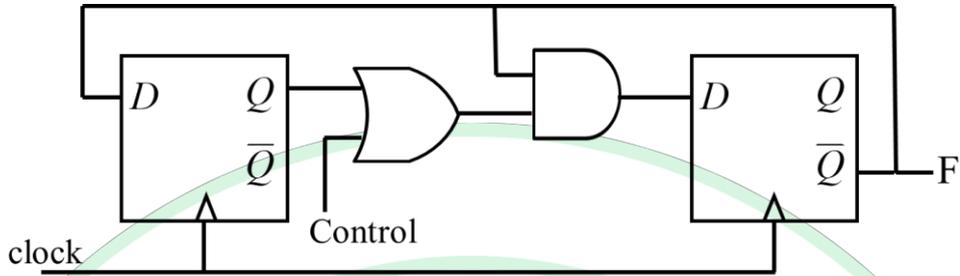
Q.40 The clock frequency of the digital circuit shown in the figure is 12 MHz. The frequencies of the output (F) corresponding to Control = 0 and Control = 1, respectively, are



- (A) 4 MHz and 6 MHz
- (B) 6 MHz and 4 MHz
- (C) 3 MHz and 4 MHz
- (D) 3 MHz and 6 MHz




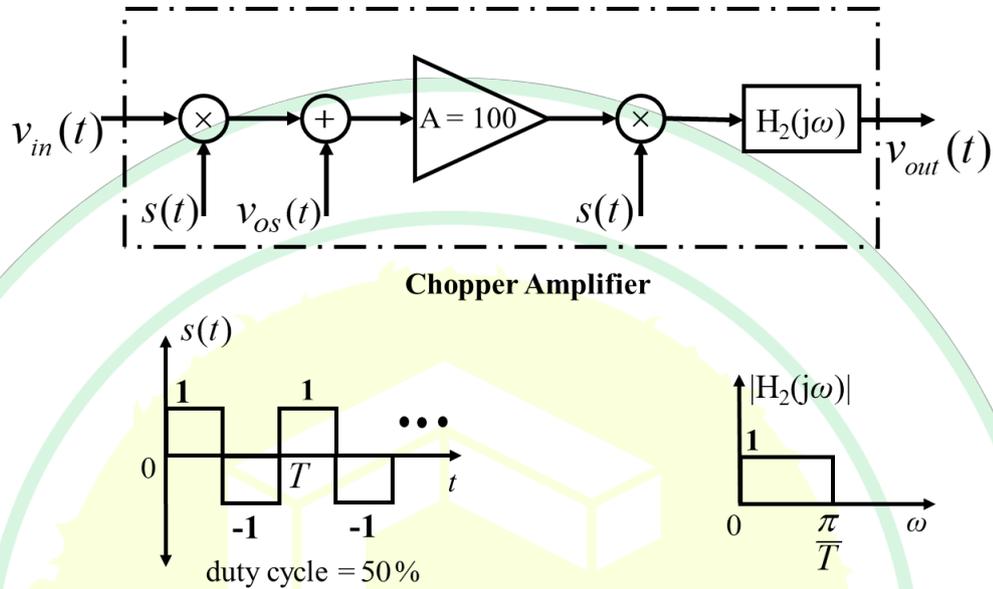Q.41 A chopper amplifier shown in the figure is designed to process a biomedical signal $v_{in}(t)$ to generate conditioned output $v_{out}(t)$. The signals $v_{in}(t)$ and $v_{os}(t)$ are band limited to 50 Hz and 10 Hz, respectively. For the system to operate as a linear amplifier, choose the correct statement from the following options.



- (A) The minimum frequency of $s(t)$ required is 100 Hz and $v_{os}(t)$ gets attenuated by the system
- (B) The minimum frequency of $s(t)$ required is 100 Hz and $v_{os}(t)$ also gets amplified by the system by a factor $\frac{200}{\pi}$
- (C) The minimum frequency of $s(t)$ required is 80 Hz and $v_{os}(t)$ gets attenuated by the system
- (D) The minimum frequency of $s(t)$ required is 80 Hz and $v_{os}(t)$ also gets amplified by the system by a factor $\frac{200}{\pi}$

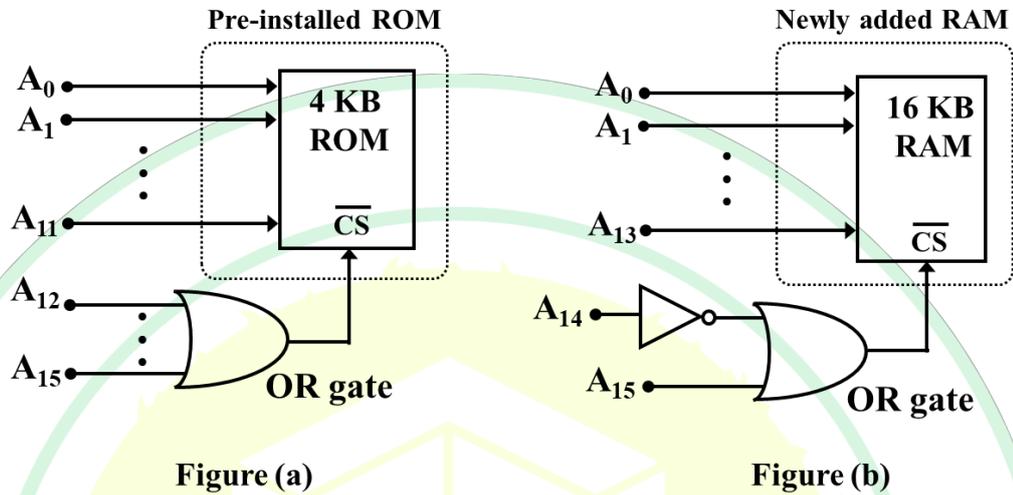
Q.42 An 8-bit microprocessor has 16-bit address bus ($A_{15} - A_0$) where A_0 is the LSB. As shown in Figure (a), it has a pre-installed 4 KB ROM whose starting address is 0000 H. The processor needs to be upgraded by adding a 16 KB RAM as shown in Figure (b). The address range for the newly added RAM is



- (A) 1000 H – 4FFF H
- (B) 3000 H – 6FFF H
- (C) 4000 H – 7FFF H
- (D) 8000 H – BFFF H



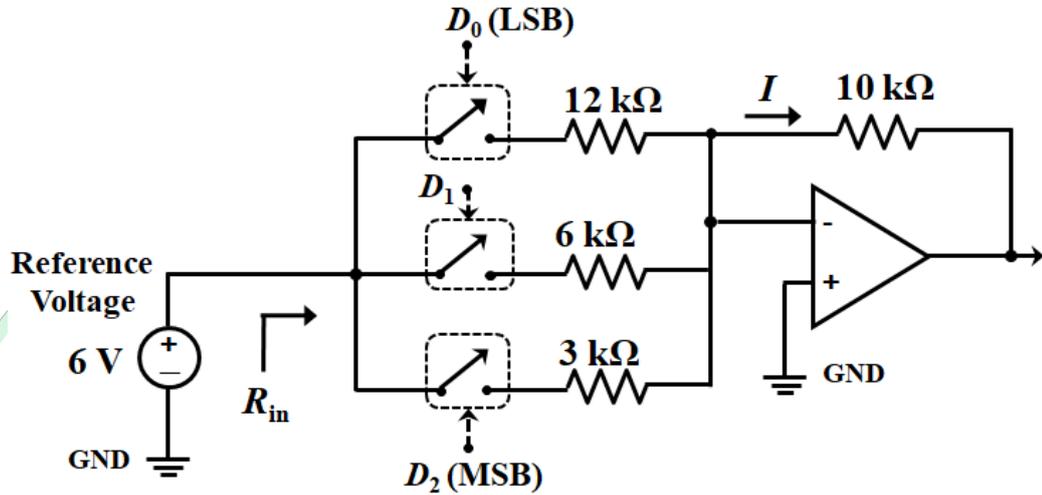Q.43 A 3-bit DAC is implemented using ideal opamp and switches as shown in the figure. Each of the switches gets closed when its corresponding digital input is at logic 1. For a digital input of 110, the resistance R_{in} seen from the reference source and the current I , are




- (A) $R_{in} = 2 \text{ k}\Omega$ and $I = 3 \text{ mA}$
- (B) $R_{in} = 12 \text{ k}\Omega$ and $I = 0.5 \text{ mA}$
- (C) $R_{in} = \infty \Omega$ and $I = 1 \text{ mA}$
- (D) $R_{in} = \infty \Omega$ and $I = 3 \text{ mA}$





Q.44	Power consumed by a three-phase balanced load is measured using two-wattmeter method. The per-phase average power drawn by the load is 30 kW at $\frac{\sqrt{3}}{2}$ lagging power factor. The readings of the wattmeters will be
(A)	15 kW and 15 kW
(B)	22.5 kW and 7.5 kW
(C)	60 kW and 30 kW
(D)	45 kW and 45 kW

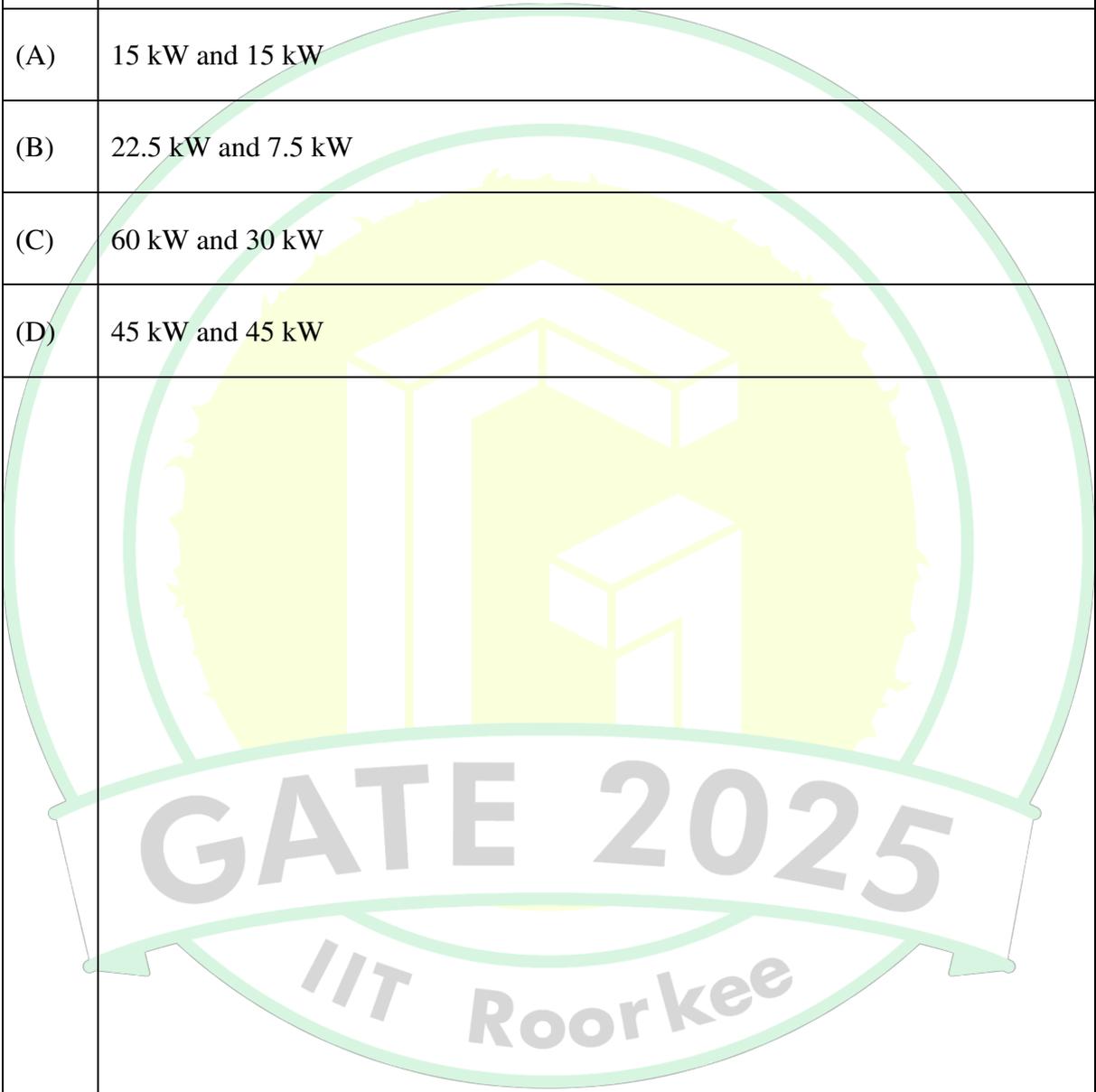

Q.45 The bridge circuit, shown in Figure (a), can be equivalently represented using the circuit shown in Figure (b). The values of R_1 , R_2 , and V_C in the equivalent circuit are

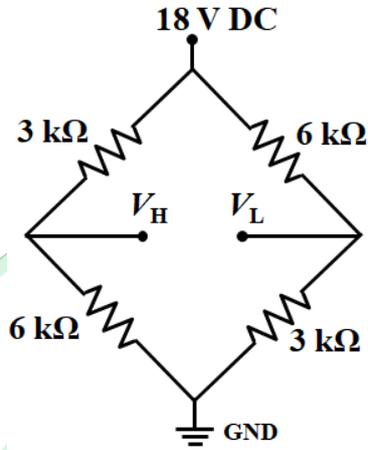


Figure (a)

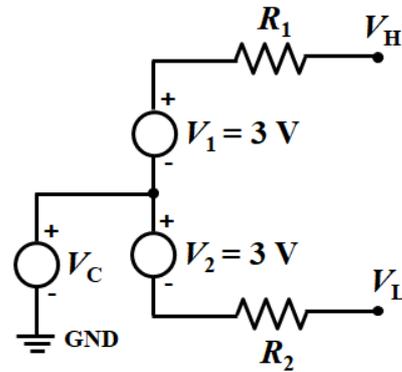


Figure (b)

- (A) $R_1 = 6 \text{ k}\Omega$, $R_2 = 3 \text{ k}\Omega$, and $V_C = 9 \text{ V}$
- (B) $R_1 = 3 \text{ k}\Omega$, $R_2 = 6 \text{ k}\Omega$, and $V_C = 4.5 \text{ V}$
- (C) $R_1 = 2 \text{ k}\Omega$, $R_2 = 2 \text{ k}\Omega$, and $V_C = 9 \text{ V}$
- (D) $R_1 = 2 \text{ k}\Omega$, $R_2 = 2 \text{ k}\Omega$, and $V_C = 4.5 \text{ V}$


GATE 2025

IIT Roorkee

Q.46	A 2-pole, 50 Hz, 3-phase induction motor supplies power to a certain load at 2970 rpm. The torque-speed curve of this machine follows a linear relationship between synchronous speed and 95 % of synchronous speed. Assume mechanical and stray losses to be zero. If the load torque of the motor is doubled, the new operating speed of the motor, in rpm, is
(A)	2940
(B)	2812
(C)	2970
(D)	2850
	

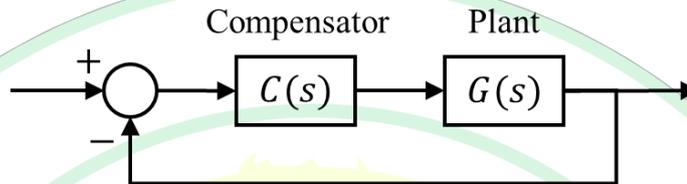Q.47


The figure shows a closed-loop system with a plant $G(s) = \frac{1}{s^2}$ and a lead compensator $C(s)$. The compensator is designed to place the dominant closed-loop poles at $-1.5 \pm j\frac{\sqrt{27}}{2}$. From the following options, choose the phase lead that the compensator needs to contribute.




- (A) 30°
- (B) 60°
- (C) 90°
- (D) 120°

GATE 2025


IIT Roorkee

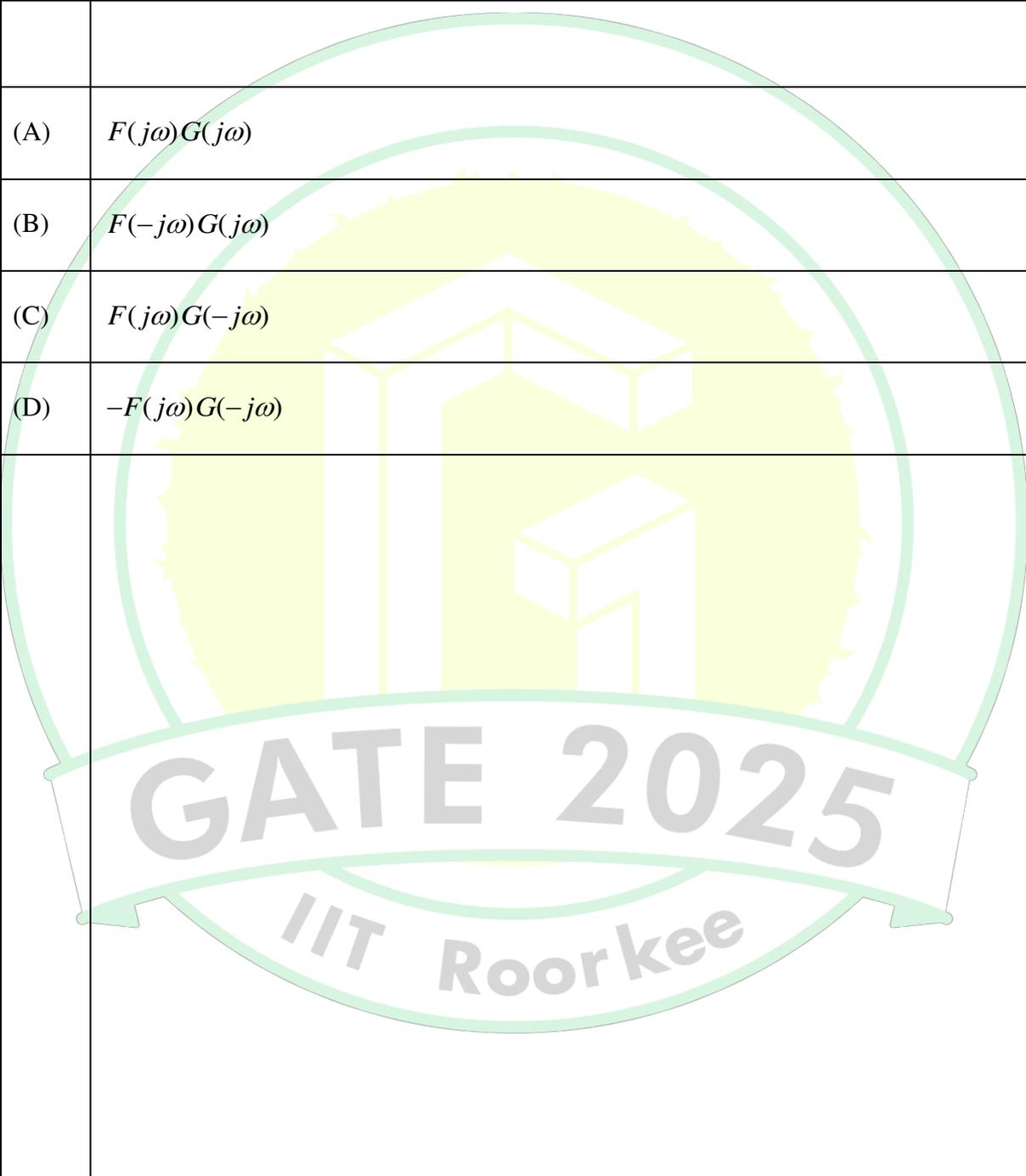Q.48	<p>Let $f(t)$ and $g(t)$ represent continuous-time real-valued signals. If $h(t)$ denotes cross-correlation between $f(t)$ and $g(-t)$, its continuous-time Fourier transform $H(j\omega)$ equals</p> <p>Note: $F(j\omega)$ and $G(j\omega)$ denote the continuous-time Fourier transforms of $f(t)$ and $g(t)$, respectively.</p>
(A)	$F(j\omega)G(j\omega)$
(B)	$F(-j\omega)G(j\omega)$
(C)	$F(j\omega)G(-j\omega)$
(D)	$-F(j\omega)G(-j\omega)$
	

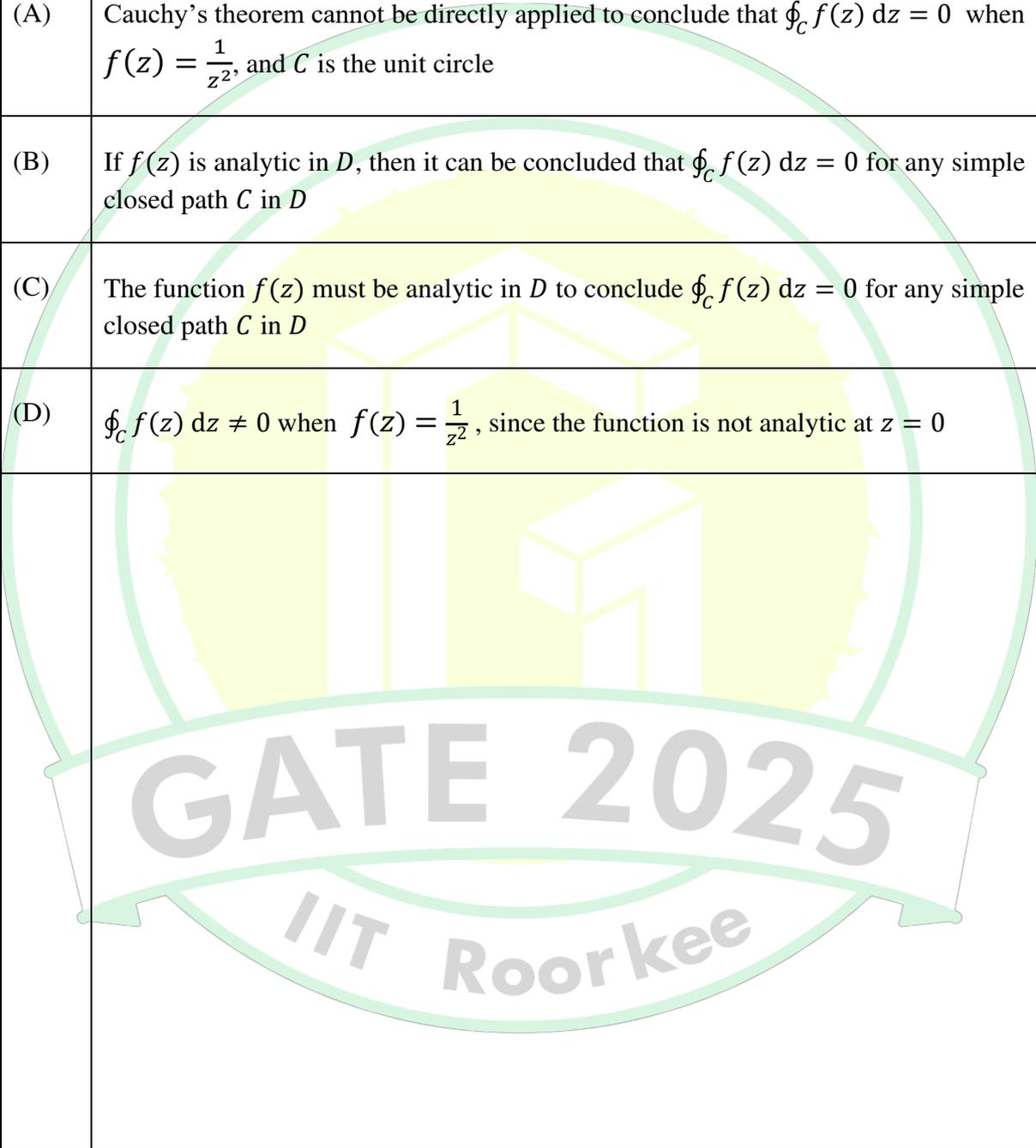Q.49	Choose the correct statement(s) from the following options, regarding Cauchy's theorem on complex integration $\oint_C f(z) dz$ where C is a simple closed path in a simply connected domain D .
(A)	Cauchy's theorem cannot be directly applied to conclude that $\oint_C f(z) dz = 0$ when $f(z) = \frac{1}{z^2}$, and C is the unit circle
(B)	If $f(z)$ is analytic in D , then it can be concluded that $\oint_C f(z) dz = 0$ for any simple closed path C in D
(C)	The function $f(z)$ must be analytic in D to conclude $\oint_C f(z) dz = 0$ for any simple closed path C in D
(D)	$\oint_C f(z) dz \neq 0$ when $f(z) = \frac{1}{z^2}$, since the function is not analytic at $z = 0$
	

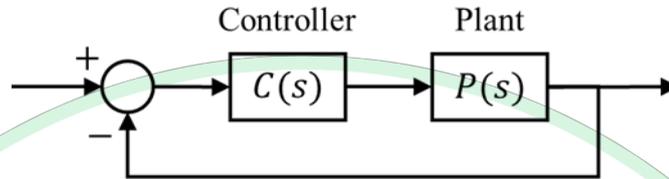Q.50

The plant in the feedback control system shown in the figure is $P(s) = \frac{a}{s^2 - b^2}$, where $a > 0$ and $b > 0$. The type(s) of controller $C(s)$ that CANNOT stabilize the plant is/are




- (A) proportional (P) controller
- (B) integral (I) controller
- (C) proportional-integral (PI) controller
- (D) proportional-derivative (PD) controller

GATE 2025

IIT Roorkee

Q. 51	Choose the eigenfunction(s) of stable linear time-invariant continuous-time systems from the following options.
(A)	$e^{j\frac{2\pi}{3}t}$
(B)	$\cos\left(\frac{2\pi}{3}t\right)$
(C)	2^t
(D)	$\sin\left(\frac{2\pi}{3}t\right)$

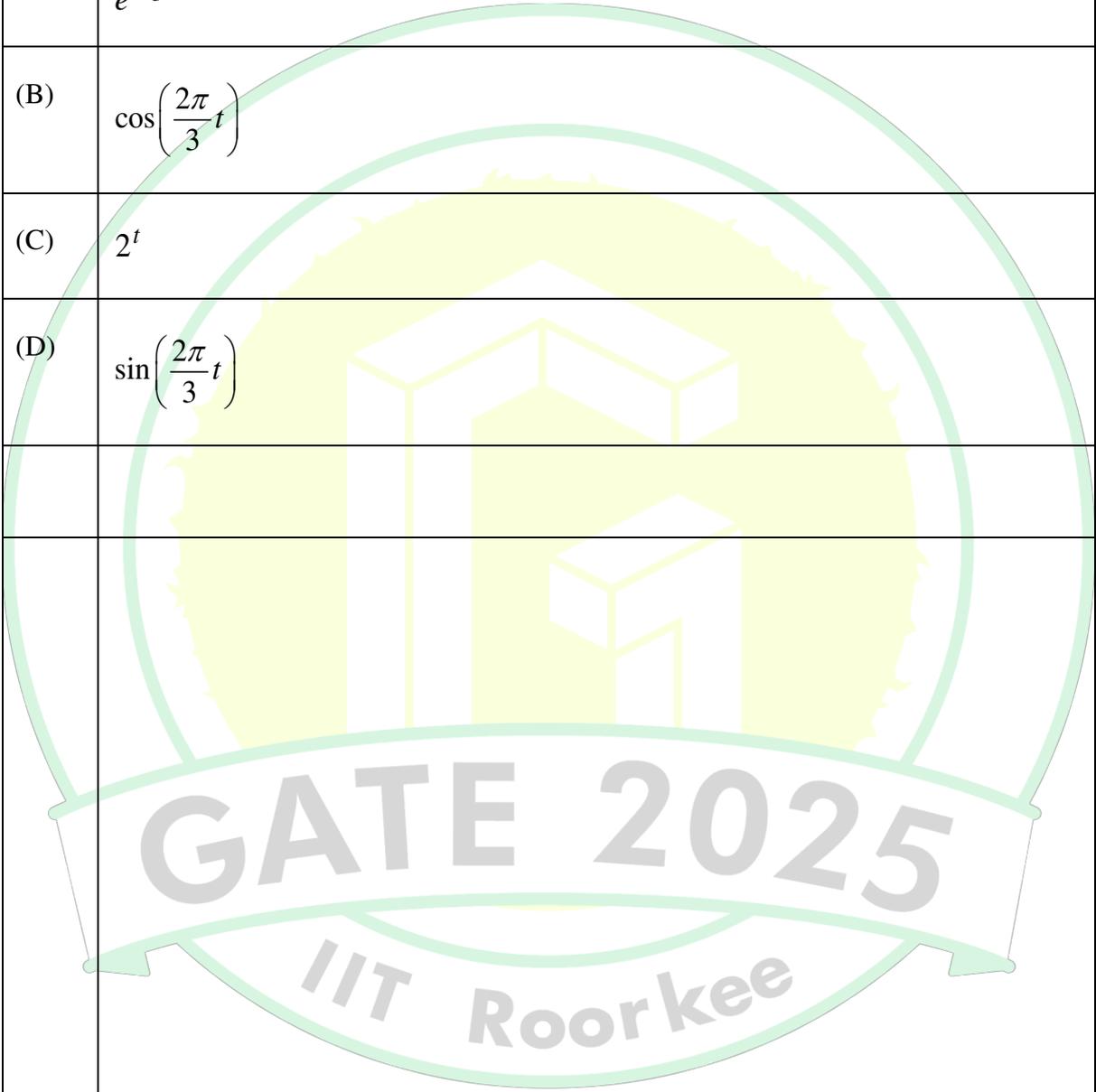

Q.52


The probability of a student missing a class is 0.1. In a total number of 10 classes, the probability that the student will not miss more than one class is ____ (**rounded off to two decimal places**).



Q.53

A metallic strain-gauge (SG) with resistance R_{SG} is connected as shown in the figure, where R_{L1} , R_{L2} , R_{L3} represent the lead wire resistances. The SG has a gauge factor of 2 and nominal resistance R_N of 125Ω . When the SG is subjected to a tensile strain of 2×10^{-3} , the resulting change in R_{SG} is ΔR . The ΔR value is measured as $\Delta R_{MEAS} = R_{EQ2} - R_{EQ1}$. The R_{EQ1} and R_{EQ2} are the equivalent resistances measured between the terminals 1 and 2, and terminals 2 and 3, respectively.

If $R_{L1} = R_{L2} = 5 \Omega$, and $R_{L3} = 4.95 \Omega$, the measured value of tensile strain is $___ \times 10^{-3}$ (rounded off to two decimal places).

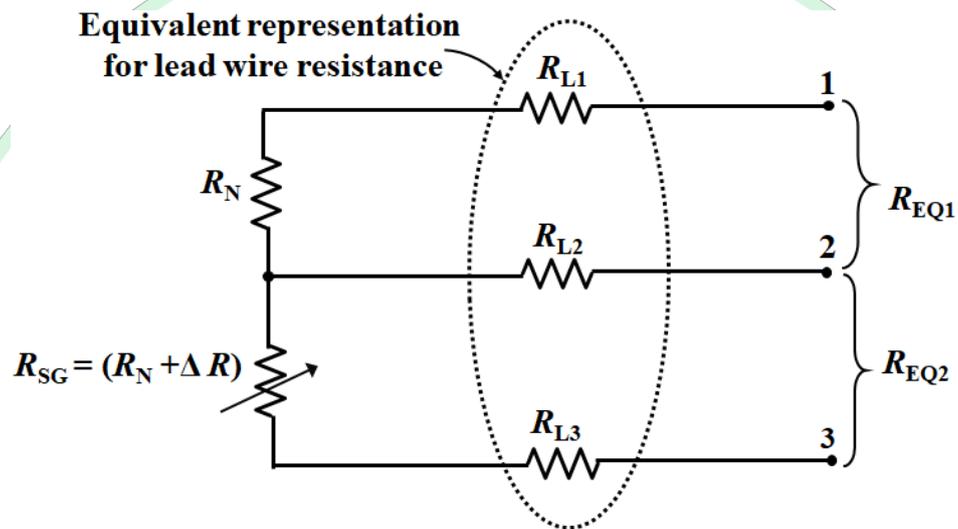

GATE 2025

IIT Roorkee

Q.54

Let $X(e^{j\omega})$ represent the discrete time Fourier transform of a 4-length sequence $x[n]$, where $x[0]=1$, $x[1]=2$, $x[2]=2$, and $x[3]=4$. $X(e^{j\omega})$ is sampled at $\omega_k = \frac{2\pi k}{3}$ to generate a periodic sequence in k with period 3, where k represents an integer. Let $y[n]$ represent another sequence such that its discrete Fourier transform $Y[k]$ is given as $Y[k]=X(e^{j\omega_k})$ for $0 \leq k \leq 2$. The value of $y[0]$ is _____ (in integer).




GATE 2025
IIT Roorkee

Q.55

A schematic of a Michelson interferometer, used for the measurement of refractive index of gas, is shown in the figure. The transparent chamber is filled with a gas of refractive index n_g , where $n_g \neq 1$, at atmospheric pressure. If a 532 nm laser beam produces 30 interference fringes on the screen, then the number of fringes produced by a 632.8 nm laser beam will be _____ (rounded off to one decimal place).

Note: Assume that the effect of beamsplitter width is negligible. The setup is placed in air medium with refractive index equal to 1.

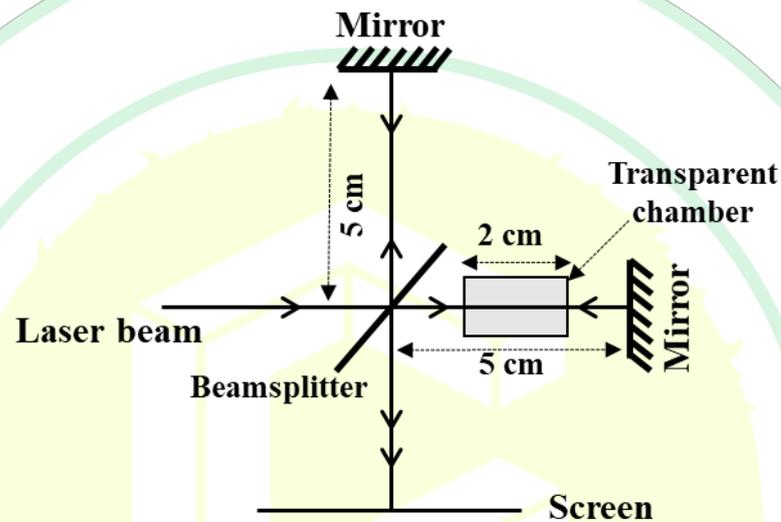


GATE 2025

IIT Roorkee

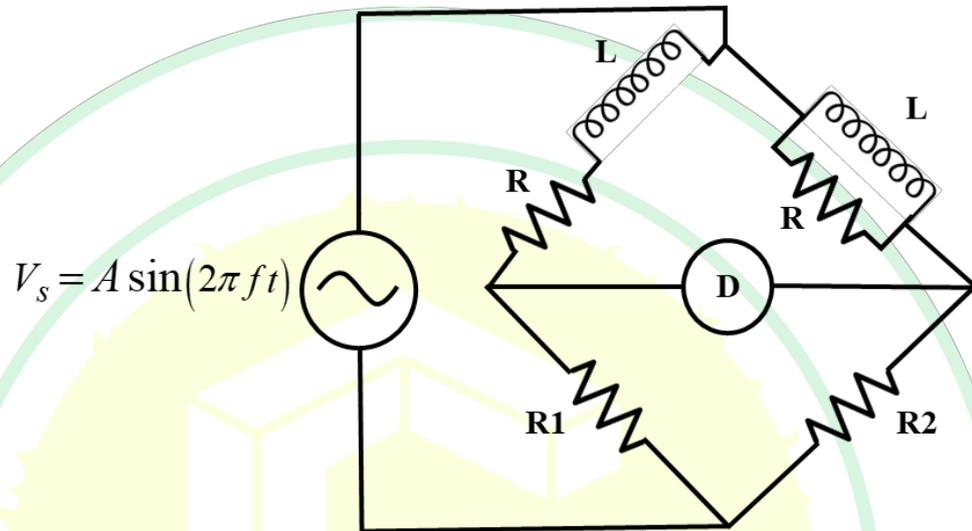Q.56


Consider an AC bridge shown in the figure with $R = 300\ \Omega$, $R_1 = 1000\ \Omega$, $R_2 = 500\ \Omega$, $L = 30\ \text{mH}$, and a detector D. At the bridge balance condition, the frequency of the excitation source V_s is _____ kHz (rounded off to two decimal places).



Q.57

An air filled parallel plate electrostatic actuator is shown in the figure. The area of each capacitor plate is $100\ \mu\text{m} \times 100\ \mu\text{m}$. The distance between the plates $d_0 = 1\ \mu\text{m}$ when both the capacitor charge and spring restoring force are zero as shown in Figure (a). A linear spring of constant $k = 0.01\ \text{N/m}$ is connected to the movable plate. When charge is supplied to the capacitor using a current source, the top plate moves as shown in Figure (b). The magnitude of minimum charge (Q) required to momentarily close the gap between the plates is $\text{_____} \times 10^{-14}\ \text{C}$ (rounded off to two decimal places).

Note: Assume a full range of motion is possible for the top plate and there is no fringe capacitance. The permittivity of free space is $\epsilon_0 = 8.85 \times 10^{-12}\ \text{F/m}$ and relative permittivity of air (ϵ_r) is 1.

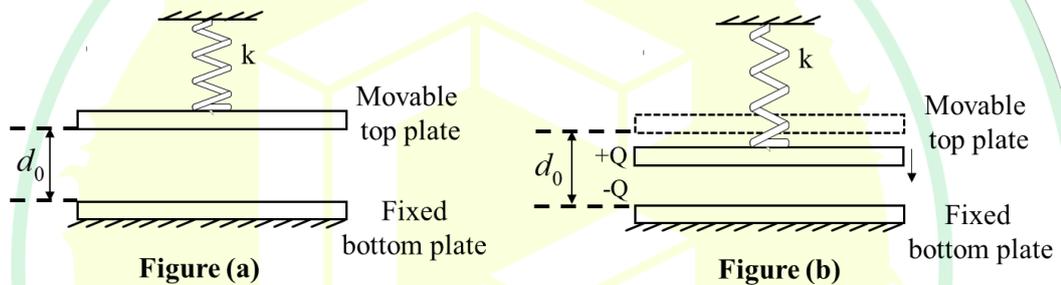

GATE 2025

IIT Roorkee




Q.58

The resistance of a thermistor is measured to be $2.25 \text{ k}\Omega$ at $30 \text{ }^\circ\text{C}$ and $1.17 \text{ k}\Omega$ at $60 \text{ }^\circ\text{C}$. Its material constant β is _____ K (rounded off to two decimal places).



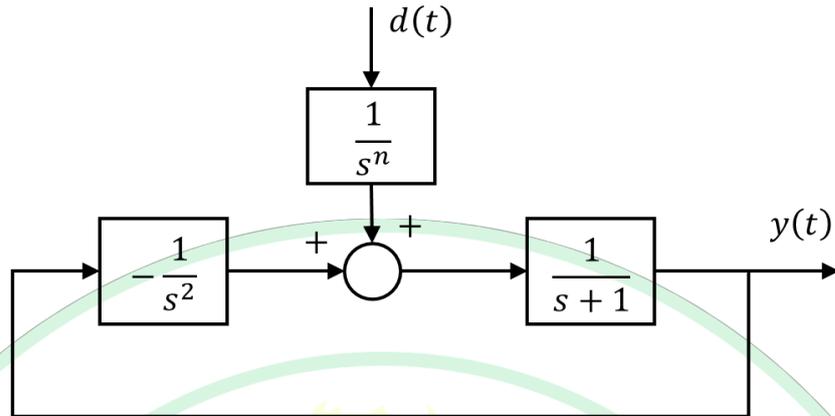Q.59

A feedback control system is shown in the figure.




The maximum allowable value of n such that the output $y(t)$, due to any step disturbance signal $d(t)$, becomes zero at steady-state, is _____ (in integer).

GATE 2025
IIT Roorkee

Q.60


The circuit given in the figure is driven by a voltage source $V_s = 25\sqrt{2}\angle 30^\circ \text{ V}$. The system is operating at a frequency of 50 Hz. The transformers are assumed to be ideal. The average power dissipated, in W, in the $50 \text{ k}\Omega$ resistance is _____ (rounded off to two decimal places).

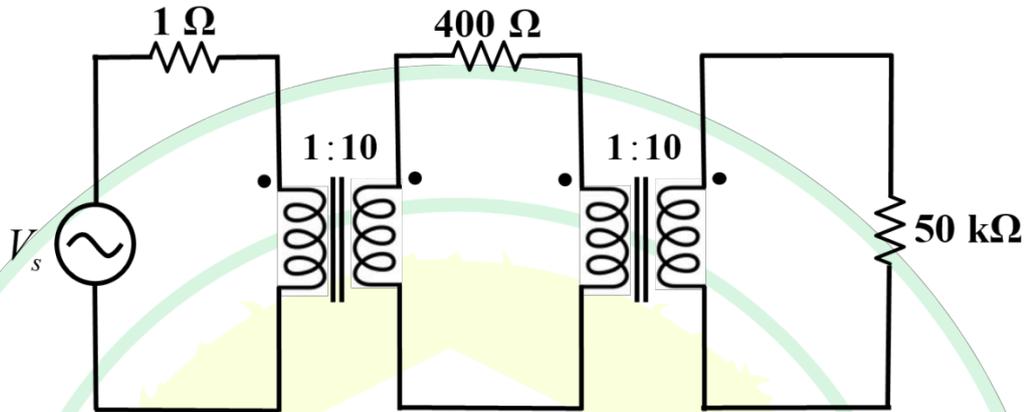

GATE 2025
IIT Roorkee

Q.61

In the circuit shown, the galvanometer (G) has an internal resistance of $100\ \Omega$. The galvanometer current I_G is _____ μA (rounded off to the nearest integer).

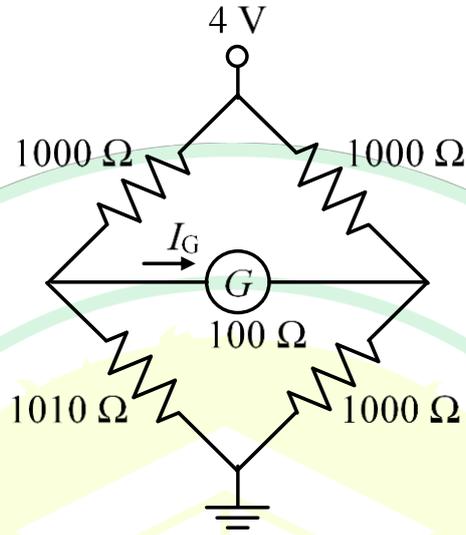

GATE 2025


IIT Roorkee



Q.62	A series RLC circuit resonates at 7500 rad/s for inductance $L = 20$ mH and resistance $R = 10 \Omega$. The uncertainties in the measurement of L and R are 0.8 mH and 0.3Ω , respectively. The percentage uncertainty in the measurement of quality factor is _____% (rounded off to one decimal place).

Q.63

In the circuit shown, the switch is opened at $t=0$ s. The current $i(t)$ at $t=2$ ms is _____ mA (rounded off to two decimal places).

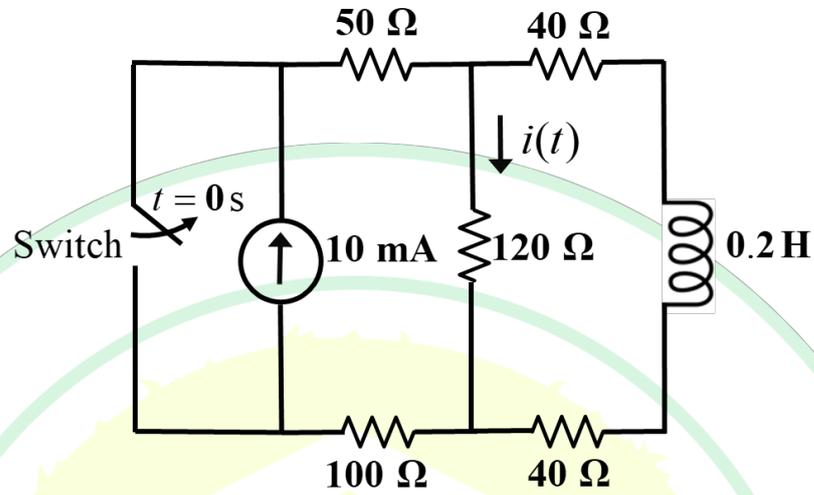


GATE 2025

IIT Roorkee

Q.64

A signal $V_M = 5\sin(\pi t/3)$ V is applied to the circuit consisting of a switch S and capacitor $C = 0.1 \mu\text{F}$, as shown in the figure. The output V_x of the circuit is fed to an ADC having an input impedance consisting of a $10 \text{ M}\Omega$ resistance in parallel with a $0.1 \mu\text{F}$ capacitor. If S is opened at $t = 0.5$ s, the value of V_x at $t = 1.5$ s will be _____ V (rounded off to two decimal places).

Note: Assume all components are ideal.

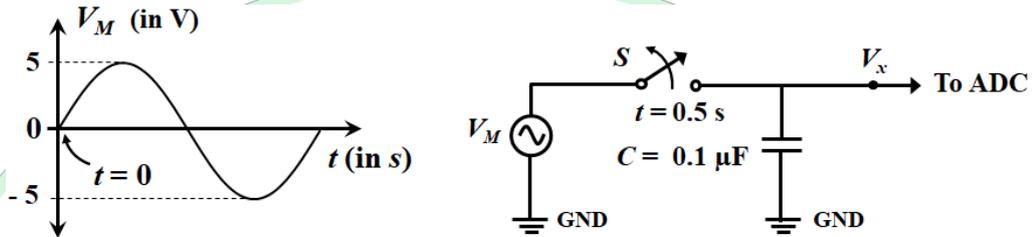


GATE 2025

IIT Roorkee

Q.65

For the circuit shown in the figure, the active power supplied by the source is _____ W (rounded off to one decimal place).

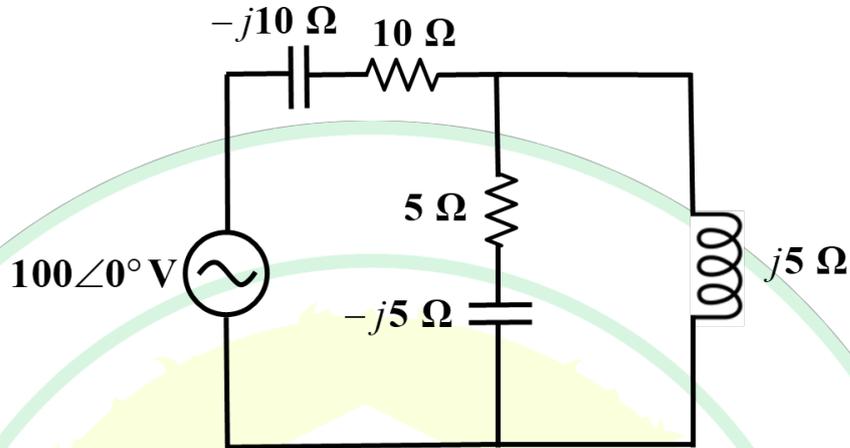

GATE 2025

IIT Roorkee