

**ISC SEMESTER 2 EXAMINATION
SPECIMEN QUESTION PAPER
ELECTRICITY AND ELECTRONICS**

Maximum Marks: 40

Time allowed: One and a half hour

Candidates are allowed an additional 10 minutes for only reading the paper.

They must NOT start writing during this time.

Answer all questions in Section A, Section B and Section C.




The intended marks for questions or parts of questions are given in brackets. []

SECTION A - 8 MARKS

Question 1

- (i) The emitter of a transistor is _____ doped (lightly, heavily) [1]
- (ii) State whether the statement given below is True or False. [1]
The value of α of a transistor is more than 1.
- (iii) Define voltage gain of a Common – Emitter (CE) amplifier. [1]
- (iv) With reference to Power Amplifier, what is meant by *impedance matching*. [1]
- (v) With reference to vacuum tubes, state the importance of *cathode bypass capacitor*. [1]
- (vi) If a triode has a mutual conductance of 1.5mA/V and plate resistance of 12K Ω , calculate its amplification factor. [1]
- (vii) The base-emitter junction of a transistor, has _____. [1]
 - (a) a reverse bias
 - (b) a wide depletion layer
 - (c) low resistance
 - (d) low conductance

(viii) Output from a transistor amplifier is: [1]

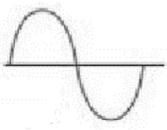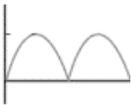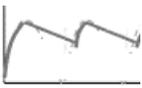- (a) 
- (b) 
- (c) 
- (d) 

SECTION B - 12 MARKS

Answer the following questions briefly.

Question 2 [2]

State *any two* differences between *half wave rectifier* and *full wave rectifier*.

Question 3 [2]

Draw a neat circuit diagram of an RC filter.

Question 4 [2]

With reference to transistors, obtain the relationship between α and β (symbols have their usual meaning).

Question 5 [2]

What inference can be drawn by maintaining control grid at:

- (i) Positive potential
- (ii) Negative potential

Question 6 [2]

State *any two* advantages of Power Amplifier over Voltage Amplifier.

Question 7

[2]

- (i) For the Common – Emitter (CE) transistor given in **Figure 1(a)**, $\beta=45$ and voltage drop across $1K\Omega$ resistor which is connected to the collector circuit is $1V$. Calculate the base current of the transistor.

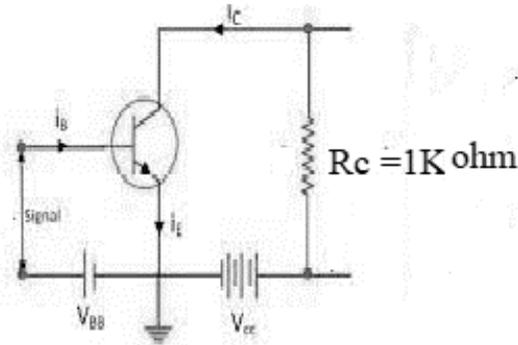


Figure 1(a)

OR

- (ii) For the Common – base (CB) transistor given in **Figure 1(b)**, the current amplification factor is 0.9 . If the emitter current is $1mA$, calculate the base current of the transistor.

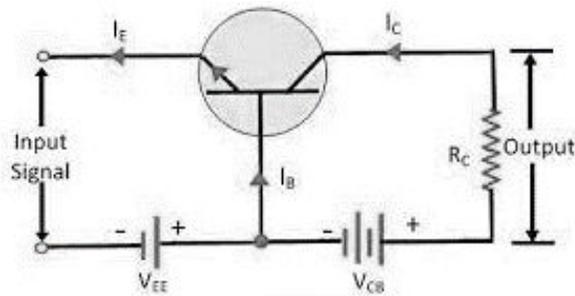


Figure 1(b)

SECTION C - 20 MARKS

Answer the following questions.

Question 8

[4]

With the help of a neat circuit diagram, explain the working of a bridge rectifier.

Question 9

[4]

With the help of a neat circuit diagram of a Common Emitter (CE) amplifier, explain how a weak signal can be amplified. (Use either PNP or NPN type of transistor)

Question 10

[4]

Figure 2 given below shows a circuit diagram of a voltage stabilizer. Explain the importance of the following:

- (i) resistor 'R'
- (ii) Zener diode

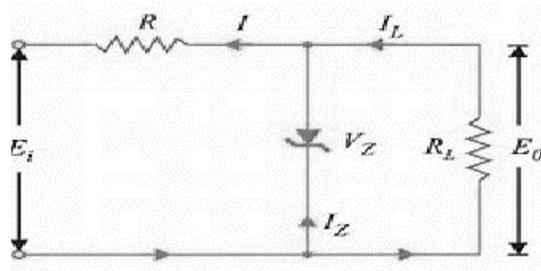


Figure 2

Question 11

[4]

- (i) Prove $I_{rms} = \frac{I_0}{\sqrt{2}}$

OR

- (ii) Prove $I_{dc} = \frac{2I_0}{\pi}$

Question 12

[4]

Explain the working of a crystal microphone. Also, state the energy conversion that takes place in this microphone.