

DAY - 17

SEAT NUMBER

--	--	--	--	--	--

2025

III

04

1100

V - 53

(E)

**ELECTRONICS
PAPER - I (C-2)**

Time : 3 Hours

4 Pages

Max. Marks : 50

- Instructions :**
- (1) All questions are compulsory.
 - (2) Figures to the right indicate full marks.
 - (3) Draw neat labelled diagrams wherever necessary.
 - (4) Use of logtable is allowed.

1. (A) Select correct alternatives from the following sub-question and rewrite the complete sentences.

(a) In a full wave bridge rectifier the ripple frequency is _____.

(i) f_m

(ii) $2 f_m$

(iii) $3 f_m$

(iv) $4 f_m$

(b) Loud Speaker is a _____ type of transducer.

(i) Pressure

(ii) Temperature

(iii) Electro acoustics

(iv) None of these

(c) In fax machines for scanning _____ are used.

(i) LEDs

(ii) LCDs

(iii) CCDs

(iv) None of these

- (d) _____ multivibrator is an oscillator.
 - (i) Astable
 - (ii) Bistable
 - (iii) Monostable
 - (iv) None of these

(B) Attempt any two of the following :

- (a) Explain the working of centre-tap full wave rectifier with neat diagram and wave-form. 3
- (b) Explain the following parameters of an operational amplifier : 3
 - (i) Input bias current
 - (ii) CMRR
 - (iii) Drift
- (c) Calculate the output pulse width for the timer used as monostable multivibrator Given, $R = 15K\Omega$ and $C = 0.22 \mu F$. Find the value of C if pulse width changes to 20 ms. 3

2. (A) Answer any two of the following :

- (a) Draw labelled diagram of Cathode Ray Tube (CRT) and explain each electrode in it. 3
- (b) Explain with the help of circuit diagram, working of Inductor input filter, when it is connected across the output terminals of a full-wave rectifier. Draw it's output wave-form. 3
- (c) Draw block diagram IC 555. Explain function of each block. 3

(B) Attempt any one of the following :

- (a) Draw a circuit diagram of an Inverting amplifier using Op-amplifier. Explain concept of virtual ground and hence derive the expression for it's output voltage. <https://www.maharashtrastudy.com> 4
- (b) What is Amplitude Modulation ? State the expression for modulated wave and draw the waveform of modulated wave. 4

3. (A) Attempt any two of the following :

- (a) With the help of Block diagram, explain the working of function Generator. 3
- (b) Draw the circuit diagram of a voltage regulator using Zener diode, explain it's working. 3
- (c) In an Op-Amp Inverting adder, $V_1 = 0.2$ volt, $V_2 = 0.1$ volt, $V_3 = 0.4$ volt, $R_1 = 1 K\Omega$, $R_2 = 2 K\Omega$, $R_3 = 4 K\Omega$. Find the output voltage if feed back resistance in $20 K\Omega$. 3

- (B) Attempt any one of the following :
- (a) Explain the working of LVDT as a transducer. Draw neat diagram. State its two applications. 4
- (b) What do you mean by Network Topology ? Explain Star, Ring and Bus Topology. 4
4. (A) Attempt any two of the following :
- (a) State any three front panel controls of CRO and give use of each control. 3
- (b) Explain with diagram and wave form working of R-C filter for reducing ripple. 3
- (c) Explain the working of differentiator circuit using operational amplifier. Derive expression for output voltage. 3
- (B) Attempt any one of the following :
- (a) Draw basic circuit for Schmitt trigger using Op-Amp. and explain the terms :
- (i) UTP 4
- (ii) LTP 4
- (iii) Hysteresis 4
- (b) Draw a block-diagram showing basic elements of a Fiber Optical Communication System. Explain function of each block in brief. 4
5. (A) Attempt any two of the following :
- (a) Explain electro-static focussing system of a CRT (Cathods Ray Tube). 3
- (b) In Full Wave Rectifier, if primary of transformer is connected to 230V, 50 Hz and secondary voltage is 12-0-12V. 3
- Calculate :
- (i) Output DC voltage
- (ii) PIV of the diode
- (iii) Output ripple frequency
- (c) Give any three advantages of FM over AM. (Frequency Modulation and Amplitude Modulation) 3
- (B) Attempt any one of the following :
- (a) State Active Transducers. Explain Optocoupler. 4
- (b) How Op-amplifier can be used as a Subtractor ? 4

OR

5. (A) Attempt **any two** of the following :
- (a) Explain the use of CRO for measurement of phase. **3**
 - (b) Explain how Op-amplifier is used as a Buffer. Draw suitable circuit diagram. **3**
 - (c) Explain how IC 555 can be used as a Pulse Position Modulator (PPM). **3**
- (B) Attempt **any one** of the following :
- (a) Explain any four characteristics of a Power Supply. **4**
 - (b) Draw general block-diagram of a pulsed radar and explain function of each block in brief. **4**
-